

HERITAGE INSTITUTE OF TECHNOLOGY



Computer Organization & Architecture Lab

CSE 2252

Lab Assignments

Stream: CSE Section: B Group :2

2nd year 2nd semester

Session: 2024 – 2025

| NAME | CLASS ROLL NUMBER | AUTONOMY ROLL NUMBER |
|--------------------|-------------------|----------------------|
| Satyam Kumar Singh | 2351097 | 12623001136 |
| Sunil Kumar Shao | 2351098 | 12623001174 |
| Smit Kumar | 2351099 | 12623001158 |
| Devayanee Gupta | 2351100 | 12623001067 |
| Shreya Denre | 2351101 | 12623001148 |
| Arijit Acharya | 2351102 | 12623001037 |

INDEX

| DAY NUMBER | TOPICS | PAGE NUMBER |
|-----------------------|--|------------------------|
| Day 1 | Basic Gates (Dataflow): AND, OR, NOT, NAND, NOR, XOR, XNOR | 3-16 |
| Day 2 | Basic Gates (Dataflow): AND, OR, NOT using Universal gates NAND, NOR | 17-28 |
| Day 3 | Basic Gates (Behavioral): AND, OR, NOT, NAND, NOR, XOR, XNOR | 29-42 |
| Day 4 | Half Adder, Full Adder, 2:1 MUX (Dataflow and Behavioral) | 43-56 |
| Day 5 | 4:1 MUX, 3:8 Decoder (Dataflow and Behavioral) 4-bit Comparator (Dataflow) | 57-69 |
| Day 6 | Behavioral Model: Arithmetic Logic Unit 8-bit Parity Checker 2's complement | 70-76 |
| Day 7 | Structural Model: Full Adder, 4-bit Ripple Carry Adder, Adder Subtractor Composite Unit, 8:1 MUX | 77-88 |
| Day 8 | Flip- Flops (Behavioral): SR, JK, D, T Shift Register (Structural) | 89-101 |
| Day 9 | Behavioral Model: 4 Bit Up Counter 4-bit Down Counter | 102-105 |


DAY 1

OR Gate (Dataflow Model)

1. VHDL Code

```
entity ord is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC);
end ord;
architecture Dataflow of ord is
begin
  c<=a OR b;
end Dataflow;
```

2. RTL Diagram

 

3. TBW Code


```
entity ord_tbw is
  -- Port ( );
end ord_tbw;
architecture Behavioral of ord_tbw is
  component ord is
    Port ( a : in STD_LOGIC;
          b : in STD_LOGIC;
          c : out STD_LOGIC);
  end component;
  Signal a1: STD_LOGIC:='0';
  Signal b1: STD_LOGIC:='0';
  Signal c1: STD_LOGIC;
begin
  uut: ord port map(a=>a1,b=>b1,c=>c1);
  stim_proc: process
```

```

begin
wait for 100 ns;
a1<='0';
b1<='0';
wait for 100 ns;
a1<='0';
b1<='1';
wait for 100 ns;
a1<='1';
b1<='0';
wait for 100 ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;

```

4.Waveform

 


AND Gate (Dataflow Model)

1. VHDL Code

```
entity andd is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC);
end andd;
architecture Dataflow of andd is
begin
  c<= a and b;
end Dataflow;
```

2.RTL Diagram

 

3.TBW Code

```
entity andd_tbw is
-- Port ( );
end andd_tbw;

architecture Behavioral of andd_tbw is
  component andd is
    Port ( a : in STD_LOGIC;
          b : in STD_LOGIC;
          c : out STD_LOGIC);
  end component;


  Signal a1 : STD_LOGIC := '0';
  Signal b1 : STD_LOGIC := '0';
  Signal c1 : STD_LOGIC;
begin
  uut: andd port map(a=>a1,b=>b1,c=>c1);
```

```

stim_proc: process
begin
wait for 100 ns;
a1<='0';
b1<='0';
wait for 100 ns;
a1<='0';
b1<='1';
wait for 100 ns;
a1<='1';
b1<='0';
wait for 100 ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;

```

4.Waveform

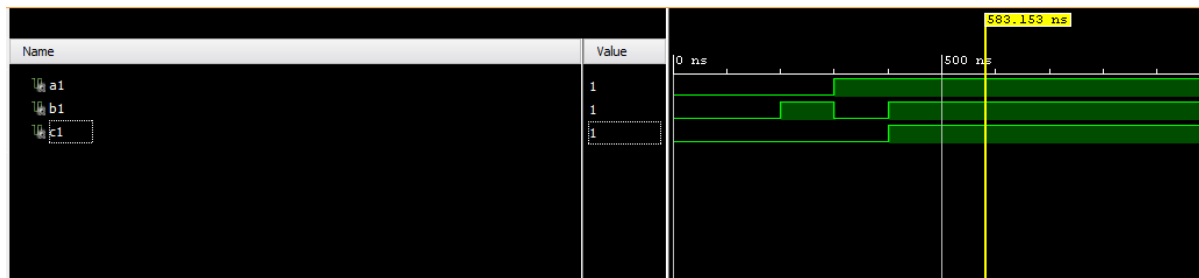


NOT Gate (Dataflow Model)

1. VHDL Code

```
entity notd is
  Port ( a : in STD_LOGIC;
        b : out STD_LOGIC);
end notd;
architecture Dataflow of notd is
begin
  b<= not a;
end Dataflow;
```

2. RTL Diagram

 


3. TBW Code

```
entity notd_tbw is
-- Port ( );
end notd_tbw;
architecture Behavioral of notd_tbw is
  component notd is
    Port ( a : in STD_LOGIC;
          b : out STD_LOGIC);
  end component;
  signal a1: STD_LOGIC:='0';
  signal b1: STD_LOGIC;
begin
  uut: notd port map(a=>a1,b=>b1);
  stim_proc: process
  begin
    wait for 100 ns;
    a1<='0';
```

```
wait for 100 ns;  
a1<='1';  
wait;  
end process;  
end Behavioral;
```

4. Waveform

 

NAND Gate (Dataflow Model)

1.VHDL Code

entity nandd is

```
Port ( a : in STD_LOGIC;  
      b : in STD_LOGIC;  
      c : out STD_LOGIC);
```

end nandd;


architecture Dataflow of nandd is

begin

```
c<=a nand b;
```

end Dataflow;

2.RTL Diagram

 

3.TBW Code

entity nandd_tbw is

```
-- Port ( );
```

end nandd_tbw;

architecture Behavioral of nandd_tbw is

component nandd is

```
Port ( a : in STD_LOGIC;  
      b : in STD_LOGIC;  
      c : out STD_LOGIC);
```

end component;

```
signal a1: STD_LOGIC:='0';
```

```
signal b1: STD_LOGIC:='0';
```

```
signal c1: STD_LOGIC;
```

begin

```
uut: nandd port map(a=>a1,b=>b1,c=>c1);
```


```
stim_proc: process
```

```

begin
wait for 100 ns;
a1<='0';
b1<='0';
wait for 100 ns;
a1<='0';
b1<='1';
wait for 100 ns;
a1<='1';
b1<='0';
wait for 100 ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;

```

4.Waveform

 

NOR Gate (Dataflow Model)

1.VHDL Code

entity nord is

```
Port ( a : in STD_LOGIC;  
      b : in STD_LOGIC;  
      c : out STD_LOGIC);
```

end nord;


architecture Dataflow of nord is

begin

```
c<=a nor b;
```

end Dataflow;

2.RTL Design

 

3.TBW Code

entity nord_tbw is

```
-- Port ( );
```

end nord_tbw;

architecture Behavioral of nord_tbw is

component nord is

```
Port ( a : in STD_LOGIC;  
      b : in STD_LOGIC;  
      c : out STD_LOGIC);
```

end component;

```
signal a1: STD_LOGIC:= '0';
```

```
signal b1: STD_LOGIC:= '0';
```

```
signal c1: STD_LOGIC;
```

begin

```
 uut: nord port map(a=>a1,b=>b1,c=>c1);
```

```
stim_proc: process
```


```
begin
```

```

wait for 100 ns;
a1<='0';
b1<='0';
wait for 100 ns;
a1<='0';
b1<='1';
wait for 100 ns;
a1<='1';
b1<='0';
wait for 100 ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;

```

4.Waveform

 

XOR Gate (Dataflow Model)

1.VHDL Code

entity xord is

```
Port ( a : in STD_LOGIC;  
      b : in STD_LOGIC;  
      c : out STD_LOGIC);
```

end xord;


architecture Dataflow of xord is

begin

```
c<=a xor b;
```

end Dataflow;

2.RTL Diagram

 

3.TBW Code

entity xord_tbw is

```
-- Port ( );
```

end xord_tbw;

architecture Behavioral of xord_tbw is

component xord is

```
Port ( a : in STD_LOGIC;  
      b : in STD_LOGIC;  
      c : out STD_LOGIC);
```

end component;

```
signal a1: STD_LOGIC:='0';
```

```
signal b1: STD_LOGIC:='0';
```

```
signal c1: STD_LOGIC;
```

begin

```
uut: xord port map(a=>a1,b=>b1,c=>c1);
```

```
stim_proc: process
```

```
begin
```

```
wait for 100 ns;
```


```
a1<='0';
```

```

b1<='0';
wait for 100 ns;
a1<='0';
b1<='1';
wait for 100 ns;
a1<='1';
b1<='0';
wait for 100 ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;

```

4.Waveform

 

XNOR Gate (Dataflow Model)

1.VHDL Code

entity xnord is

```
Port ( a : in STD_LOGIC;  
      b : in STD_LOGIC;  
      c : out STD_LOGIC);
```

end xnord;


architecture Dataflow of xnord is

begin

```
c<=a xnor b;
```

end Dataflow;

2.RTL Design

 

3.TBW Code

entity xnord_tbw is

```
-- Port ( );
```

end xnord_tbw;

architecture Behavioral of xnord_tbw is

component xnord is

```
Port ( a : in STD_LOGIC;  
      b : in STD_LOGIC;  
      c : out STD_LOGIC);
```

end component;

```
signal a1: STD_LOGIC:='0';
```

```
signal b1: STD_LOGIC:='0';
```

```
signal c1: STD_LOGIC;
```

begin

```
uut: xnord port map(a=>a1,b=>b1,c=>c1);
```


```
stim_proc: process
```

```

begin
wait for 100 ns;
a1<='0';
b1<='0';
wait for 100 ns;
a1<='0';
b1<='1';
wait for 100 ns;
a1<='1';
b1<='0';
wait for 100 ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;

```

4.Waveform

 


DAY 2

AND Gate using NAND Gates (Dataflow Model)

1. VHDL Code

```
entity and_nandd is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC);
end and_nandd;
architecture Dataflow of and_nandd is
begin
  c<=(a nand b) nand (a nand b);
end Dataflow;
```

2. RTL Design

 

3.TBW Code

```
entity and_nandtbw is
-- Port ( );
end and_nandtbw;
architecture Behavioral of and_nandtbw is
  component and_nandd is
    Port ( a : in STD_LOGIC;
          b : in STD_LOGIC;
          c : out STD_LOGIC);
  end component;
  signal a1: STD_LOGIC:='0';
  signal b1: STD_LOGIC:='0';
  signal c1: STD_LOGIC;
begin
  uut: and_nandd port map(a=>a1,b=>b1,c=>c1);
  stim_proc: process
  begin
    wait for 100 ns;
    a1<='0';
```


```

b1<='0';
wait for 100 ns;
a1<='0';
b1<='1';
wait for 100 ns;
a1<='1';
b1<='0';
wait for 100 ns;
a1<='1';
b1<='1';
wait;

end process;
end Behavioral;

```

4. Waveform

 


OR Gate using NAND Gates (Dataflow Model)

1. VHDL Code

```
entity or_nandd is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC);
end or_nandd;
architecture Dataflow of or_nandd is
begin
  c<=(a nand a) nand (b nand b);
end Dataflow;
```

2. RTL Design

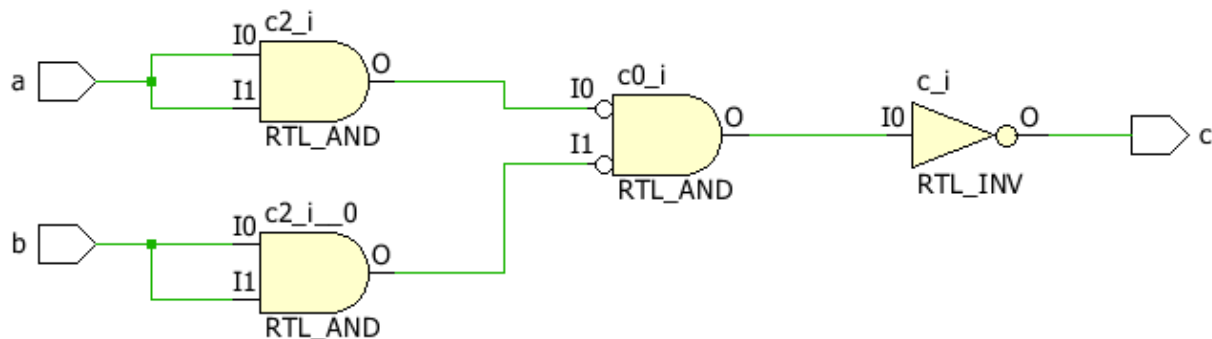

3. TBW Code

```
entity or_nandtbw is
  -- Port ( );
end or_nandtbw;

architecture Behavioral of or_nandtbw is

  component or_nandd is
    Port ( a : in STD_LOGIC;
          b : in STD_LOGIC;
          c : out STD_LOGIC);
  end component;

  signal a1: STD_LOGIC:= '0';
  signal b1: STD_LOGIC:= '0';
  signal c1: STD_LOGIC;

begin
  uut: or_nandd port map(a=>a1,b=>b1,c=>c1);
  stim_proc: process
```


```

begin
wait for 100 ns;
a1<='0';
b1<='0';
wait for 100 ns;
a1<='0';
b1<='1';
wait for 100 ns;
a1<='1';
b1<='0';
wait for 100 ns;
a1<='1';
b1<='1';
wait;
end process;

```

end Behavioral;

4. Waveform

 


NOT Gate using NAND Gates (Dataflow Model)

1. VHDL Code

```
entity not_nandd is
  Port ( a : in STD_LOGIC;
        b : out STD_LOGIC);
end not_nandd;
```

```
architecture Dataflow of not_nandd is
begin
  b<=a nand a;
end Dataflow;
```


2. RTL Design

 

3. TBW Code

```
entity not_nandtbw is
-- Port ( );
end not_nandtbw;
architecture Behavioral of not_nandtbw is
  component not_nandd is
    Port ( a : in STD_LOGIC;
          b : out STD_LOGIC);
  end component;
  signal a1:STD_LOGIC:='0';
  signal b1:STD_LOGIC;
begin
  uut: not_nandd port map (a=>a1,b=>b1);
  stim_proc: process
  begin
    wait for 100ns;
    a1<='0';
    wait for 100 ns;
    a1<='1';
    wait;
  end process;
end Behavioral;
```

4. Waveform

 

AND Gate using NOR Gates (Dataflow Model)

1. VHDL Code

entity and_nord is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC);

end and_nord;


architecture Dataflow of and_nord is

begin

c<=(a nor a) nor (b nor b);

end Dataflow;

2. RTL Design

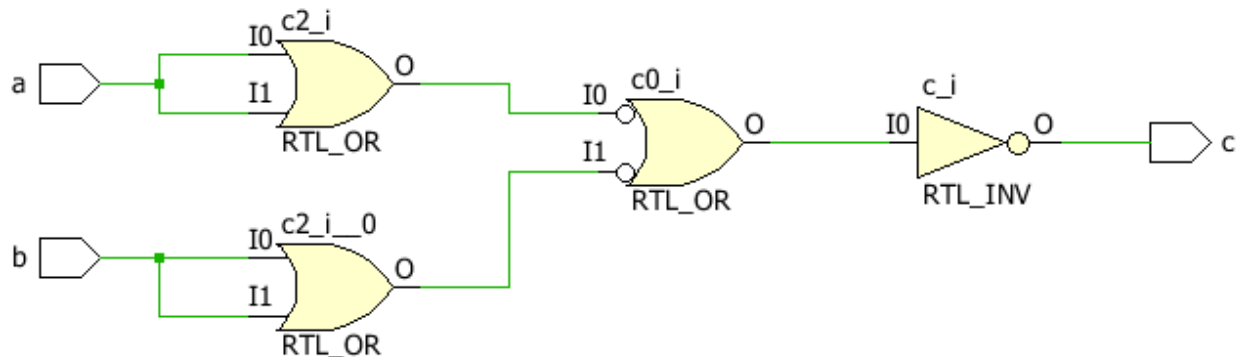

3. TBW Code

entity and_nortbw is

-- Port ();

end and_nortbw;

architecture Behavioral of and_nortbw is

component and_nord is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC);

end component;

signal a1: STD_LOGIC:='0';

signal b1: STD_LOGIC:='0';

signal c1: STD_LOGIC;

begin

uut: and_nord port map(a=>a1,b=>b1,c=>c1);


stim_proc: process

```

begin
wait for 100 ns;
a1<='0';
b1<='0';
wait for 100 ns;
a1<='0';
b1<='1';
wait for 100 ns;
a1<='1';
b1<='0';
wait for 100 ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;

```

4. Waveform

 


OR Gate using NOR Gates (Dataflow Model)

1. VHDL Code

```
entity or_nord is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC);
end or_nord;
```

```
architecture Dataflow of or_nord is
begin
  c<=(a nor b) nor ( a nor b);
end Dataflow;
```

2. RTL Design

 

3. TBW Code

```
entity or_nortbw is
-- Port ( );
end or_nortbw;
```

```
architecture Behavioral of or_nortbw is
component or_nord is
```

```
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC);
end component;
signal a1: STD_LOGIC:='0';
signal b1: STD_LOGIC:='0';
signal c1: STD_LOGIC;
begin
  uut: or_nord port map(a=>a1,b=>b1,c=>c1);
  stim_proc: process
  begin
    wait for 100 ns;
    a1<='0';
    b1<='0';
    wait for 100 ns;
```


```

a1<='0';
b1<='1';
wait for 100 ns;
a1<='1';
b1<='0';
wait for 100 ns;
a1<='1';
b1<='1';
wait;
end process;

```

end Behavioral;

4. Waveform

 


NOT Gate using NOR Gates (Dataflow Model)

1. VHDL Code

```
entity not_nord is
  Port ( a : in STD_LOGIC;
        b : out STD_LOGIC);
end not_nord;
architecture Dataflow of not_nord is
begin
  b<=a nor a;
end Dataflow;
```

2. RTL Design

 


3. TBW Code

```
entity not_nortbw is
-- Port ( );
end not_nortbw;

architecture Behavioral of not_nortbw is
  component not_nord is
    Port ( a : in STD_LOGIC;
          b : out STD_LOGIC);
  end component;
  signal a1:STD_LOGIC:='0';
  signal b1:STD_LOGIC;
begin
  uut: not_nord port map (a=>a1,b=>b1);
  stim_proc: process
  begin
```

```
wait for 100ns;  
a1<='0';  
wait for 100 ns;  
a1<='1';  
wait;  
end process;  
end Behavioral;
```

4. Waveform

 


DAY 3

AND Gate (Behavioral Model)

1.VHDL Code

```
entity and_bv is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC);
end and_bv;
architecture Behavioral of and_bv is
begin
  process(a,b)
  begin
    if(a='1'and b='1')then
      c<='1';
    else
      c<='0';
    end if;
  end process;
end Behavioral;
```

2.RTL Design

 

3.TBW Code


```
entity and_bvtbw is
-- Port ( );
end and_bvtbw;
architecture Behavioral of and_bvtbw is
  component and_bv is
    Port ( a : in STD_LOGIC;
          b : in STD_LOGIC;
          c : out STD_LOGIC);
  end component;
  Signal a1 : STD_LOGIC := '0';
  Signal b1 : STD_LOGIC := '0';
  Signal c1 : STD_LOGIC;
begin
```

```

    uut: and_bv port map(a=>a1,b=>b1,c=>c1);
    stim_proc: process
    begin
        wait for 100 ns;
        a1<='0';
        b1<='0';
        wait for 100 ns;
        a1<='0';
        b1<='1';
        wait for 100 ns;
        a1<='1';
        b1<='0';
        wait for 100 ns;
        a1<='1';
        b1<='1';
        wait;
    end process;
end Behavioral;

```

4.Waveform

 


OR Gate (Behavioral Model)

1.VHDL Code

```
entity or_bv is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC);
end or_bv;
architecture Behavioral of or_bv is
begin
  process(a,b)
  begin
    if(a='1' or b='1') then
      c<='1';
    else
      c<='0';
    end if;
  end process;
end Behavioral;
```

2.RTL Design

 

3.TBW Code

```
entity or_bvtbw is
-- Port ( );
end or_bvtbw;


architecture Behavioral of or_bvtbw is
  component or_bv is
    Port ( a : in STD_LOGIC;
          b : in STD_LOGIC;
          c : out STD_LOGIC);
  end component;
  Signal a1: STD_LOGIC:= '0';
```

```

Signal b1: STD_LOGIC:='0';
Signal c1: STD_LOGIC;
begin
uut: or_bv port map(a=>a1,b=>b1,c=>c1);
stim_proc: process
begin
wait for 100 ns;
a1<='0';
b1<='0';
wait for 100 ns;
a1<='0';
b1<='1';
wait for 100 ns;
a1<='1';
b1<='0';
wait for 100 ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;

```

4.Waveform

 

NOT Gate (Behavioral Model)


1.VHDL Code

```
entity not_bv is
  Port ( a : in STD_LOGIC;
        b : out STD_LOGIC);
end not_bv;

architecture Behavioral of not_bv is
```

```
begin
  process(a)
  begin
    if(a='1')then
      b<='0';
    else
      b<='1';
    end if;
  end process;
```

2.RTL Design

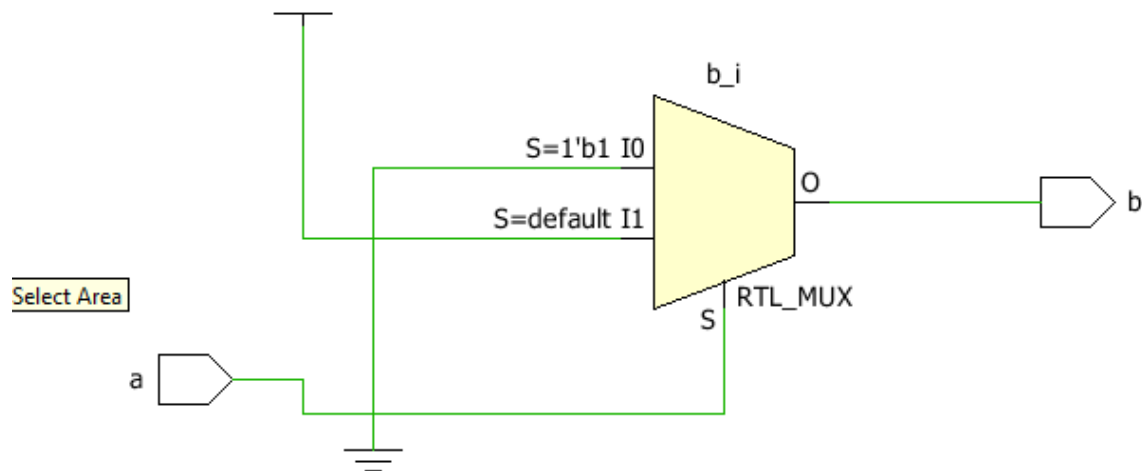

3.TBW Code

```
entity not_bvtbw is
  -- Port ( );
end not_bvtbw;
```

```
architecture Behavioral of not_bvtbw is
  component not_bv is
    Port ( a : in STD_LOGIC;
```


```

        b : out STD_LOGIC);
end component;
signal a1: STD_LOGIC:='0';
signal b1: STD_LOGIC;
begin
uut: not_bv port map(a=>a1,b=>b1);
stim_proc: process
begin
wait for 100 ns;
a1<='0';

wait for 100 ns;
a1<='1';
wait;
end process;
end Behavioral;

```

4.Waveform

 


NOR Gate (Behavioral Model)

1.VHDL Code

```
entity nor_bv is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC);
end nor_bv;
architecture Behavioral of nor_bv is
begin
  process(a,b)
  begin
    if(a = '0' and b = '0') then
      c <= '1';
    else
      c <= '0';
    end if;
  end process;
end Behavioral;
```

2.RTL Design

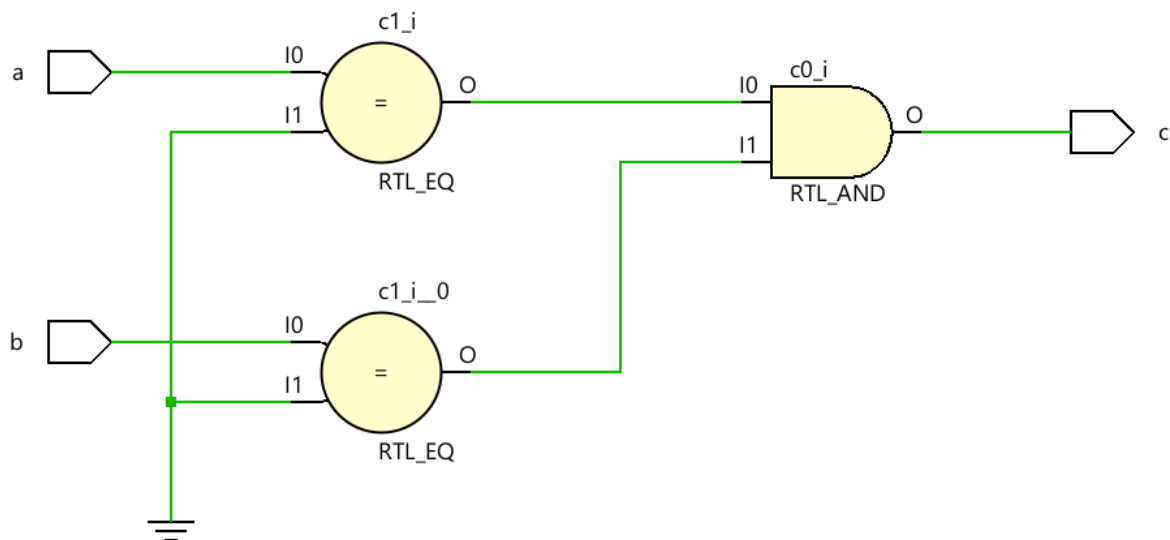

3.TBW Code


```
entity nor_bvrbw is
  -- Port ( );
end nor_bvrbw;
```

```

architecture Behavioral of nor_bvtbw is
component nor_bv is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC);
end component;
signal a1: STD_LOGIC:='0';
signal b1: STD_LOGIC:='0';
signal c1: STD_LOGIC;
begin
  uut: nor_bv port map(a=>a1,b=>b1,c=>c1);
  stim_proc: process
  begin
    wait for 100 ns;
    a1<='0';
    b1<='0';
    wait for 100 ns;
    a1<='0';
    b1<='1';
    wait for 100 ns;
    a1<='1';
    b1<='0';
    wait for 100 ns;
    a1<='1';
    b1<='1';
    wait;
  end process;
end Behavioral;

```

4.Waveform

 


NAND Gate (Behavioral Model)

1.VHDL Code

```
entity nand_bv is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC);
end nand_bv;
architecture Behavioral of nand_bv is
begin
  process(a,b)
  begin
    if(a = '1' and b = '1') then
      c <= '0';
    else
      c <= '1';
    end if;
  end process;
end Behavioral;
```

2.RTL Design

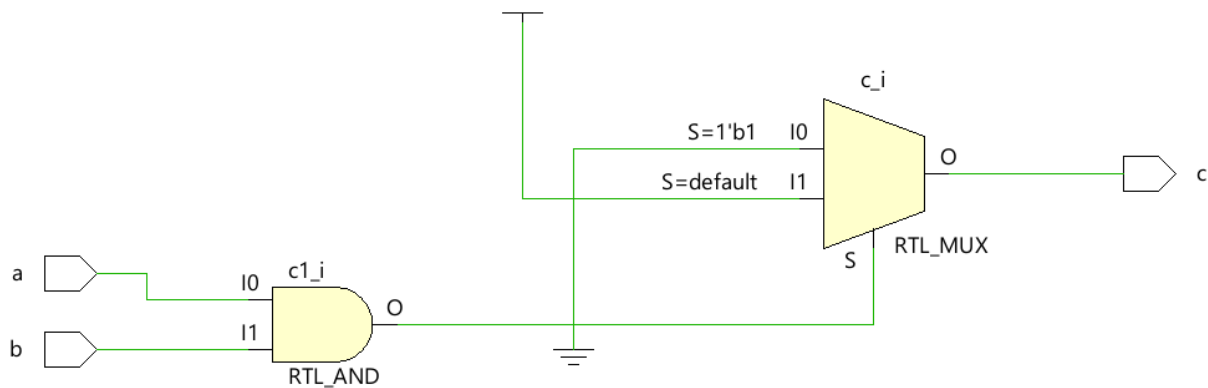

3.TBW Code

```
entity nand_bv_tbw is
-- Port ( );
end nand_bv_tbw;


architecture Behavioral of nand_bv_tbw is
  component nand_bv is
    Port ( a : in STD_LOGIC;
```

```

        b : in STD_LOGIC;
        c : out STD_LOGIC);
end component;
signal a1: STD_LOGIC:='0';
signal b1: STD_LOGIC:='0';
signal c1: STD_LOGIC;
begin
uut: nand_bv port map(a=>a1,b=>b1,c=>c1);
stim_proc: process
begin
wait for 100 ns;
a1<='0';
b1<='0';
wait for 100 ns;
a1<='0';
b1<='1';
wait for 100 ns;
a1<='1';
b1<='0';
wait for 100 ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;

```

4.Waveform

 

XOR Gate (Behavioral Model)

1.VHDL Code


```
entity xor_bv is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC);
end xor_bv;

architecture Behavioral of xor_bv is

begin
  process(a,b)
  begin
    if(a=b)then
      c<='0';
    else
      c<='1';
    end if;
  end process;

end Behavioral;
```

2.RTL Design

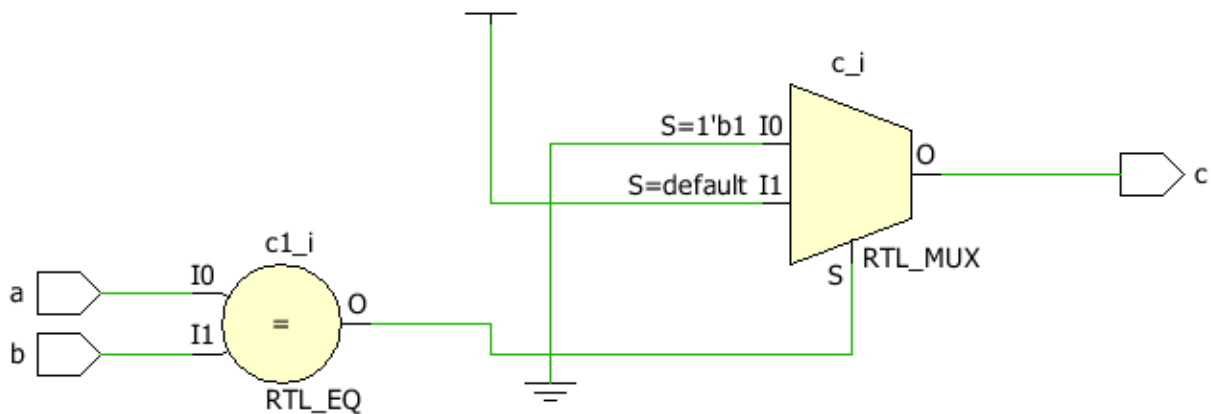

3.TBW Code


```
entity xor_bvtbw is
  -- Port ( );
end xor_bvtbw;
```

```

architecture Behavioral of xor_bvtbw is
component xor_bv is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC);
end component;
signal a1: STD_LOGIC:= '0';
signal b1: STD_LOGIC:= '0';
signal c1: STD_LOGIC;
begin
  uut: xor_bv port map(a=>a1,b=>b1,c=>c1);
  stim_proc: process
  begin
    wait for 100 ns;
    a1<='0';
    b1<='0';
    wait for 100 ns;
    a1<='0';
    b1<='1';
    wait for 100 ns;
    a1<='1';
    b1<='0';
    wait for 100 ns;
    a1<='1';
    b1<='1';
    wait;
  end process;
end Behavioral;

```

4.Waveform

 


XNOR Gate (Behavioral Model)

1.VHDL Code

```
entity xnor_bv is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC);
end xnor_bv;
architecture Behavioral of xnor_bv is
begin
  process(a,b)
  begin
    if(a=b)then
      c<='1';
    else
      c<='0';
    end if;
  end process;
end Behavioral;
```

2.RTL Design

 

3.TBW Code

```
entity xnor_bvtbw is
  -- Port ( );
end xnor_bvtbw;


architecture Behavioral of xnor_bvtbw is
  component xnor_bv is
    Port ( a : in STD_LOGIC;
          b : in STD_LOGIC;
```

```

        c : out STD_LOGIC);
end component;
signal a1: STD_LOGIC:= '0';
signal b1: STD_LOGIC:= '0';
signal c1: STD_LOGIC;
begin
    uut: xnor_bv port map(a=>a1,b=>b1,c=>c1);
    stim_proc: process
    begin
        wait for 100 ns;
        a1<='0';
        b1<='0';
        wait for 100 ns;
        a1<='0';
        b1<='1';
        wait for 100 ns;
        a1<='1';
        b1<='0';
        wait for 100 ns;
        a1<='1';
        b1<='1';
        wait;
    end process;
end Behavioral;

```

4.Waveform

 


DAY 4

Half-Adder (Dataflow Model)

1.VHDL Code

```
entity half_adder_df is
  Port ( x : in STD_LOGIC;
        y : in STD_LOGIC;
        s : out STD_LOGIC;
        c : out STD_LOGIC);
end half_adder_df;
architecture Dataflow of half_adder_df is
begin
  s<= x xor y;
  c<= x and y;
end Dataflow;
```

2.RTL Design

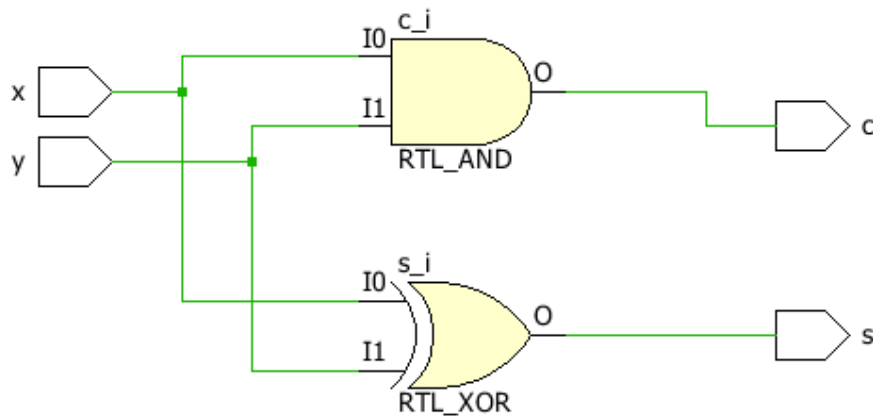

3.TBW Code

```
entity half_adderdf_tbw is
-- Port ( );
end half_adderdf_tbw;


architecture Behavioral of half_adderdf_tbw is
  component half_adderdf is
    Port ( x : in STD_LOGIC;
          y : in STD_LOGIC;
          s : out STD_LOGIC;
          c : out STD_LOGIC);
  end component;
  signal x1: STD_LOGIC:='0';
  signal y1: STD_LOGIC:='0';
```

```

signal s1: STD_LOGIC;
signal c1: STD_LOGIC;
begin
 uut: half_adderdf port map(x=>x1,y=>y1,s=>s1,c=>c1);
 stim_proc: process
 begin
 wait for 100 ns;
 x1<='0';
 y1<='0';
 wait for 100 ns;
 x1<='0';
 y1<='1';
 wait for 100 ns;
 x1<='1';
 y1<='0';
 wait for 100 ns;
 x1<='1';
 y1<='1';
 wait;
 end process;
end Behavioral;

```

4.Waveform

 

Half-Adder (Behavioral Model)

1.VHDL Code

entity half_addf is

Port (x : in STD_LOGIC;

y : in STD_LOGIC;

s : out STD_LOGIC;

c : out STD_LOGIC);

end half_addf;

architecture Behavioral of half_addf is

begin

process(x,y)

begin

if(x=y)then

s<='0';

else

s<='1';

end if;

if(x='1' and y='1')then

c<='1';

else


c<='0';

end if;

end process;

end Behavioral;

2.RTL Design

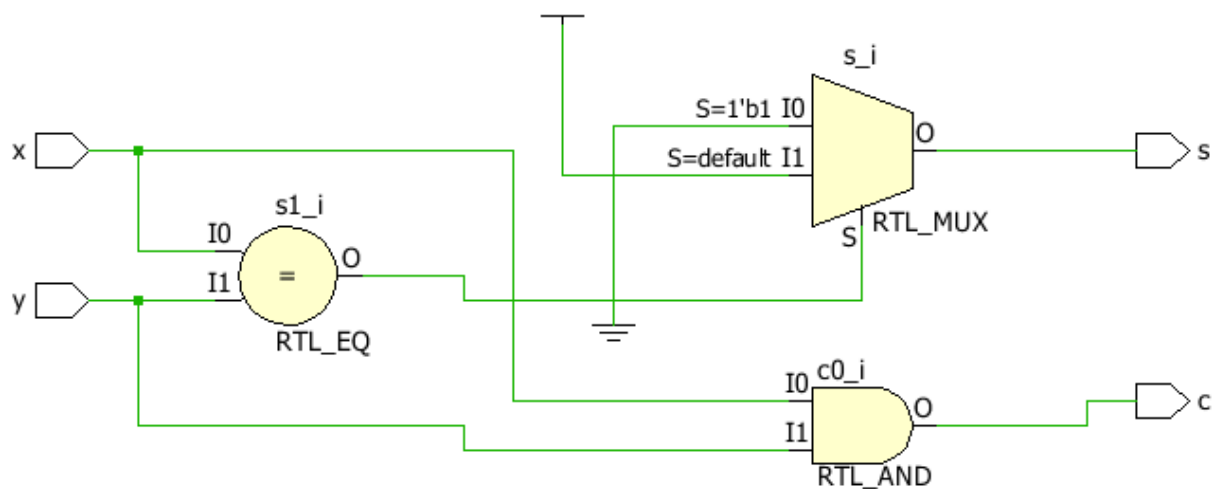

3.TBW Code


```

entity half_addf_tbw is
-- Port ( );
end half_addf_tbw;

architecture Behavioral of half_addf_tbw is
component half_addf is
    Port ( x : in STD_LOGIC;
          y : in STD_LOGIC;
          s : out STD_LOGIC;
          c : out STD_LOGIC);
end component;
signal x1: STD_LOGIC:='0';
signal y1: STD_LOGIC:='0';
signal s1: STD_LOGIC;
signal c1: STD_LOGIC;
begin
    uut: half_addf port map(x=>x1,y=>y1,s=>s1,c=>c1);
    stim_proc: process
    begin
        wait for 100 ns;
        x1<='0';
        y1<='0';
        wait for 100 ns;
        x1<='0';
        y1<='1';
        wait for 100 ns;
        x1<='1';
        y1<='0';
        wait for 100 ns;
        x1<='1';
        y1<='1';
        wait;
    end process;
end Behavioral;

```

4.Waveform

 

Full-Adder (Dataflow Model)

1.VHDL Code

entity full_adder_df is

Port (x : in STD_LOGIC;

 y : in STD_LOGIC;

 z : in STD_LOGIC;

 s : out STD_LOGIC;

 c : out STD_LOGIC);

end full_adder_df;

architecture Dataflow of full_adder_df is


begin

s<=(x xor y) xor z;

c<=(x and y) or (x and z) or (y and z);

end Dataflow;

2.RTL Design

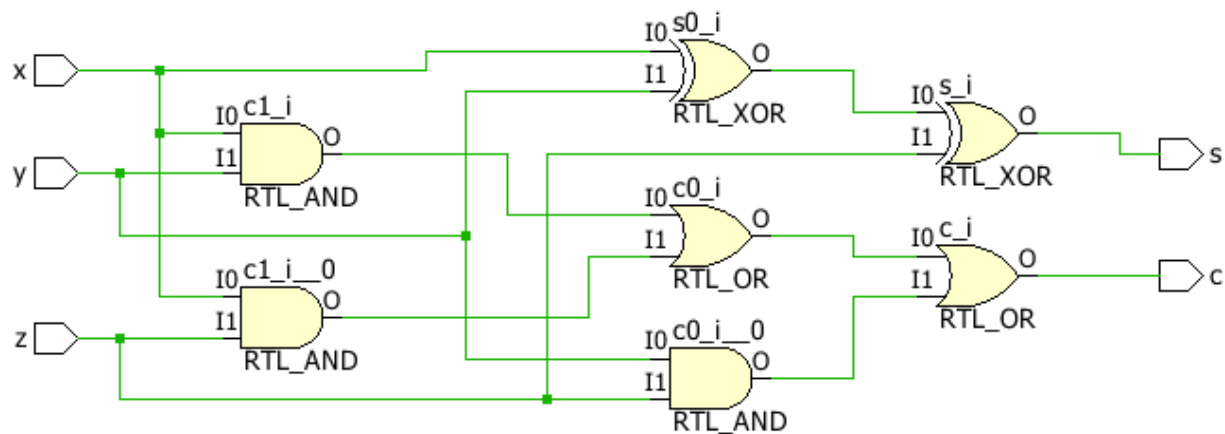

3.TBW Code

entity full_adder_dftbw is

-- Port ();

end full_adder_dftbw;

architecture Behavioral of full_adder_dftbw is

component full_adder_df is

Port (x : in STD_LOGIC;

 y : in STD_LOGIC;

```

        z : in STD_LOGIC;
        s : out STD_LOGIC;
        c : out STD_LOGIC);
end component;
signal x1: STD_LOGIC:='0';
signal y1: STD_LOGIC:='0';
signal z1: STD_LOGIC:='0';
signal s1: STD_LOGIC;
signal c1: STD_LOGIC;
begin
uut: full_adder_df port map(x=>x1,y=>y1,z=>z1,s=>s1,c=>c1);
stim_proc: process
begin
wait for 50 ns;
x1<='0';
y1<='0';
z1<='0';
wait for 50 ns;
x1<='0';
y1<='0';
z1<='1';
wait for 50 ns;
x1<='0';
y1<='1';
z1<='0';
wait for 50 ns;
x1<='0';
y1<='1';
z1<='1';
wait for 50 ns;
x1<='1';
y1<='0';
z1<='0';
wait for 50 ns;
x1<='1';
y1<='0';
z1<='1';
wait for 50 ns;
x1<='1';
y1<='1';
z1<='0';
wait for 50 ns;
x1<='1';

```



```

y1<='1';
z1<='1';
wait;
end process;
end Behavioral;

```

4.Waveform



Full-Adder (Behavioral Model)

1.VHDL Code


```
entity full_adder_bv is
  Port ( x : in STD_LOGIC;
        y : in STD_LOGIC;
        z : in STD_LOGIC;
        s : out STD_LOGIC;
        c : out STD_LOGIC);
end full_adder_bv;
```

architecture Behavioral of full_adder_bv is

```
begin
  process(x,y,z)
  begin
    if(x='0')then
      if(y=z)then
        s<='0';
      else
        s<='1';
      end if;
    if(y='1' and z='1')then
      c<='1';
    else
      c<='0';
    end if;
  end if;
```

```
--second half
  if(x='1')then
    if(y=z)then
      s<='1';
    else
      s<='0';
    end if;
  if(y='1' or z='1')then
    c<='1';
  else
    c<='0';
```

2.RTL Design

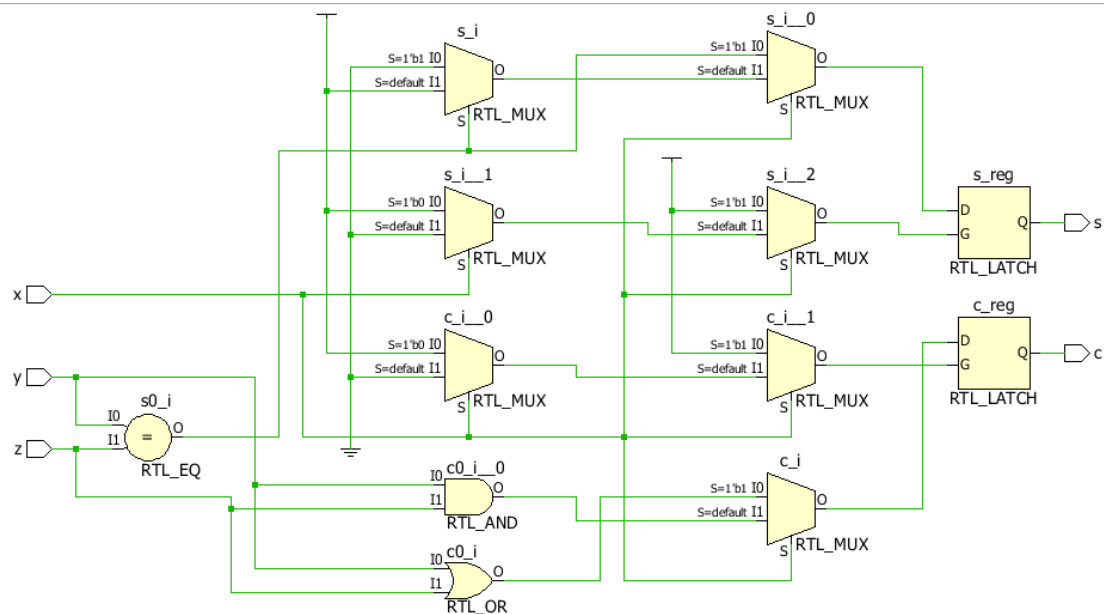

3.TBW Code

entity full_adder_bvtbw is

```
-- Port ( );
```

```
end full_adder_bvtbw;
```

architecture Behavioral of full_adder_bvttbw is

component full_adder_bv is

Port (x : in STD_LOGIC;

```
y : in STD_LOGIC;
```

```
z : in STD_LOGIC;
```

```
s : out STD_LOGIC;
```

```
c : out STD_LOGIC);
```

end component;

```
signal x1: STD_LOGIC:='0';
```

```
signal y1: STD_LOGIC:='0';
```

```
signal z1: STD_LOGIC:='0';
```

```
signal s1: STD_LOGIC;
```

```
signal c1: STD_LOGIC;
```

begin

```
uut: full_adder_bv port map(x=>x1,y=>y1,z=>z1,s=>s1,c=>c1);
```

stim_proc: process

begin

```
wait for 50 ns;
```

```

x1<='0';
y1<='0';
z1<='0';
wait for 50 ns;
x1<='0';
y1<='0';
z1<='1';
wait for 50 ns;
x1<='0';
y1<='1';
z1<='0';
wait for 50 ns;
x1<='0';
y1<='1';
z1<='1';
wait for 50 ns;
x1<='1';
y1<='0';
z1<='0';
wait for 50 ns;
x1<='1';
y1<='0';
z1<='1';
wait for 50 ns;
x1<='1';
y1<='1';
z1<='0';
wait for 50 ns;
x1<='1';
y1<='1';
z1<='1';
wait;
end process;
end Behavioral;

```

4.Waveform



2:1 MUX (Dataflow Model)

1.VHDL Code

entity mux2_1 is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC;

s : in STD_LOGIC);

end mux2_1;


architecture Dataflow of mux2_1 is

begin

c<=((not s) and a) or (s and b);

end Dataflow;

2.RTL Design

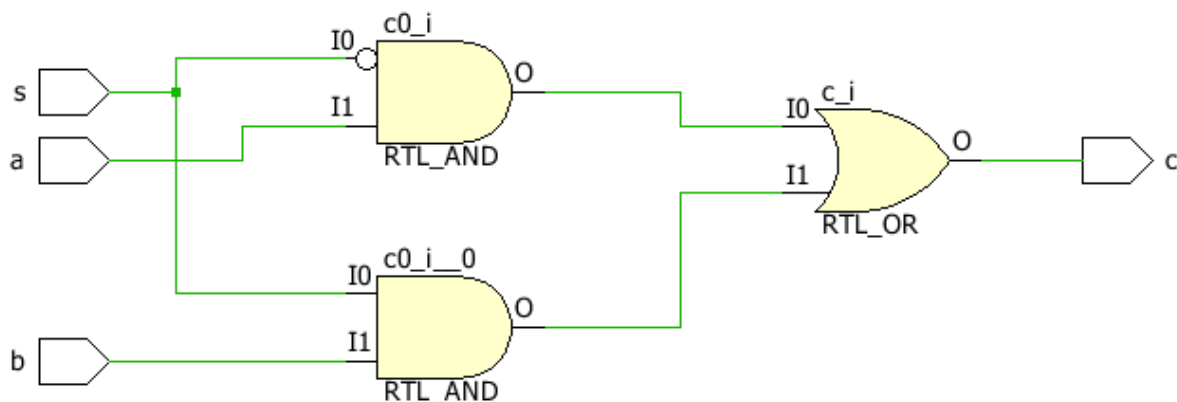

3.TBW Code

entity mux2_1_tbw is

-- Port ();

end mux2_1_tbw;

architecture Behavioral of mux2_1_tbw is

component mux2_1 is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC;

s : in STD_LOGIC);

```

end component;
signal a1: STD_LOGIC:='0';
signal b1: STD_LOGIC:='1';
signal s1: STD_LOGIC:='0';
signal c1: STD_LOGIC;
begin
  uut: mux2_1 port map(a=>a1,b=>b1,c=>c1,s=>s1);
  stim_proc: process
  begin
    wait for 100ns;
    s1<='0';

    wait for 100ns;
    s1<='1';

    wait;
  end process;
end Behavioral;

```

4.Waveform



2:1 MUX (Behavioral Model)

1.VHDL Code

entity mux2_1_bv is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC;

s : in STD_LOGIC);

end mux2_1_bv;

architecture Behavioral of mux2_1_bv is

begin

process(a,b,s)

begin

if(s='0')then

c<=a;

else


c<=b;

end if;

end process;

end Behavioral;

2.RTL Design

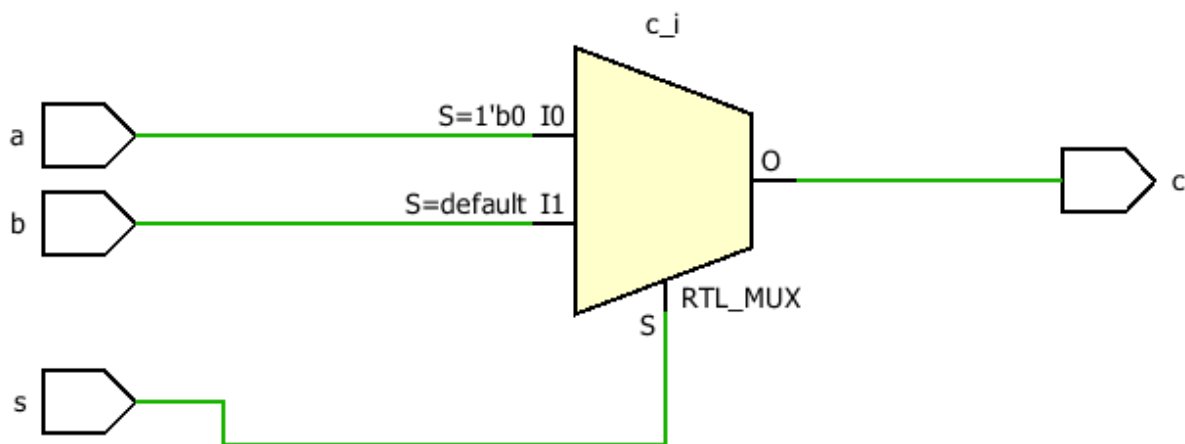

3.TBW Code

entity mux2_1_bvtbw is

-- Port ();

end mux2_1_bvtbw;

```

architecture Behavioral of mux2_1_bv is
component mux2_1_bv is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC;
        s : in STD_LOGIC);
end component;
signal a1: STD_LOGIC:='0';
signal b1: STD_LOGIC:='1';
signal s1: STD_LOGIC:='0';
signal c1: STD_LOGIC;
begin
  uut: mux2_1_bv port map(a=>a1,b=>b1,c=>c1,s=>s1);
  stim_proc: process
  begin
    wait for 100ns;
    s1<='0';

    wait for 100ns;
    s1<='1';

    wait;
  end process;
end Behavioral;

```

4.Waveform




DAY 5

4:1 MUX (Dataflow Model)

1.VHDL Code

```
entity mux4_1_df is
  Port ( ip : in STD_LOGIC_VECTOR (3 downto 0);
        sel : in STD_LOGIC_VECTOR (1 downto 0);
        y : out STD_LOGIC);
end mux4_1_df;
architecture Dataflow of mux4_1_df is
begin
  y<=ip(0) when sel="00" else
  ip(1) when sel="01" else
  ip(2) when sel="10" else
  ip(3);
end Dataflow;
```

2.RTL Design

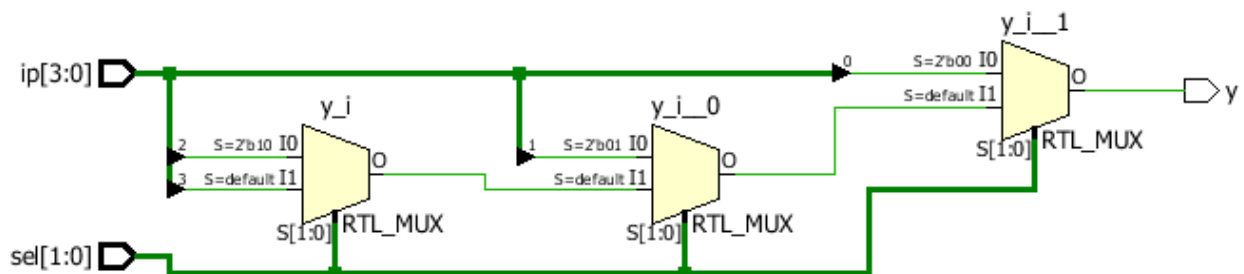

3.TBW Code

```
entity mux4_1_dftbw is
  -- Port ( );
end mux4_1_dftbw;


architecture Behavioral of mux4_1_dftbw is
  component mux4_1_df is
    Port ( ip : in STD_LOGIC_VECTOR (3 downto 0);
          sel : in STD_LOGIC_VECTOR (1 downto 0);
          y : out STD_LOGIC);
  end component;
  Signal ip1: STD_LOGIC_VECTOR(3 downto 0):="0101";
```

```

Signal sel1: STD_LOGIC_VECTOR(1 downto 0):="00";
Signal y1:STD_LOGIC;
begin
uut: mux4_1_df port map(ip=>ip1,sel=>sel1,y=>y1);
stim_proc: process
begin
wait for 100ns;
sel1<="00";
wait for 100ns;
sel1<="01";
wait for 100ns;
sel1<="10";
wait for 100ns;
sel1<="11";
wait;
end process;
end Behavioral;

```

4.Waveform

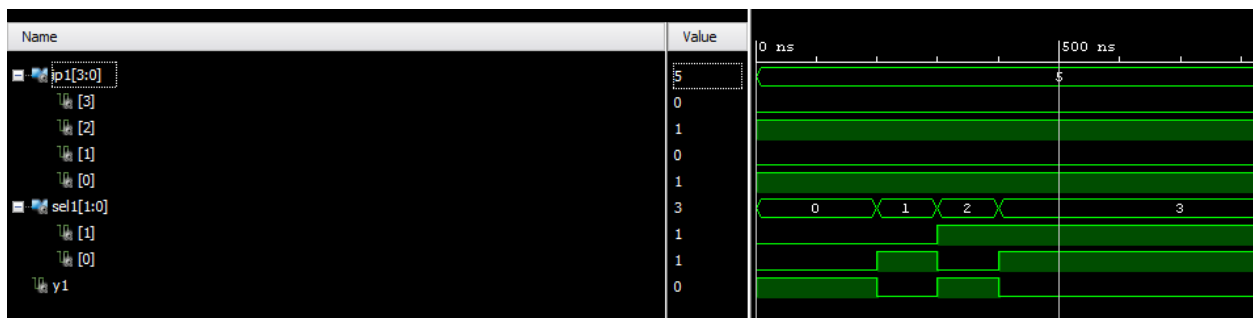

4:1 MUX (Behavioral Model)


1.VHDL Code

```
entity mux4_1_bv is
  Port ( ip : in STD_LOGIC_VECTOR (3 downto 0);
        sel : in STD_LOGIC_VECTOR (1 downto 0);
        y : out STD_LOGIC);
end mux4_1_bv;
```

architecture Behavioral of mux4_1_bv is

```
begin
  process(ip,sel)
  begin
    case sel is
      when "00" => y <= ip(0);
      when "01" => y <= ip(1);
      when "10" => y <= ip(2);
      when "11" => y <= ip(3);
      when others=>NULL;
    end case;
  end process;
end Behavioral;
```

2.RTL Design

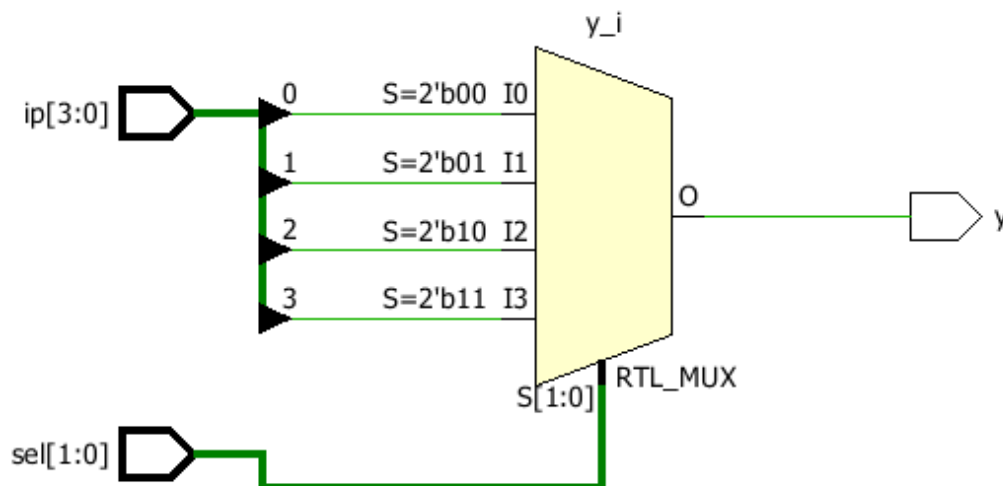

3.TBW Code

```
entity mux4_1_bvtbw is
```


```

-- Port ( );
end mux4_1_bvbw;

architecture Behavioral of mux4_1_bvbw is
component mux4_1_bv is
    Port ( ip : in STD_LOGIC_VECTOR (3 downto 0);
          sel : in STD_LOGIC_VECTOR (1 downto 0);
          y : out STD_LOGIC);
end component;
Signal ip1: STD_LOGIC_VECTOR(3 downto 0):="0101";
Signal sel1: STD_LOGIC_VECTOR(1 downto 0):="00";
Signal y1:STD_LOGIC;
begin
    uut: mux4_1_bv port map(ip=>ip1,sel=>sel1,y=>y1);
    stim_proc: process
    begin
        wait for 100ns;
        sel1<="00";
        wait for 100ns;
        sel1<="01";
        wait for 100ns;
        sel1<="10";
        wait for 100ns;
        sel1<="11";
        wait;
    end process;
end Behavioral;

```

4.Waveform

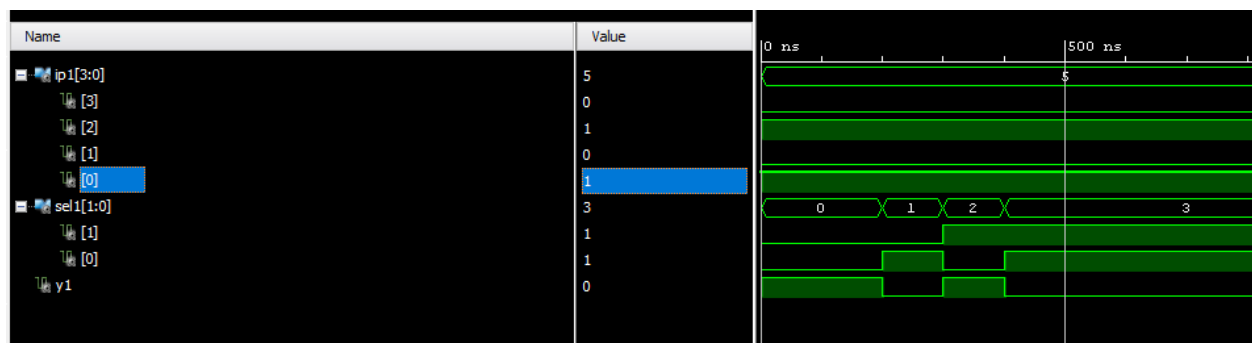


3:8 decoder (Dataflow Model)

1.VHDL Code

```
entity decoder3_8_df is
  Port ( ip : in STD_LOGIC_VECTOR (2 downto 0);
        op : out STD_LOGIC_VECTOR (7 downto 0));
end decoder3_8_df;
architecture Dataflow of decoder3_8_df is
begin
  op(0)<='1' when ip="000" else '0';
  op(1)<='1' when ip="001" else '0';
  op(2)<='1' when ip="010" else '0';
  op(3)<='1' when ip="011" else '0';
  op(4)<='1' when ip="100" else '0';
  op(5)<='1' when ip="101" else '0';
  op(6)<='1' when ip="110" else '0';
  op(7)<='1'when ip="111" else '0';
end Dataflow;
```

2.RTL Design

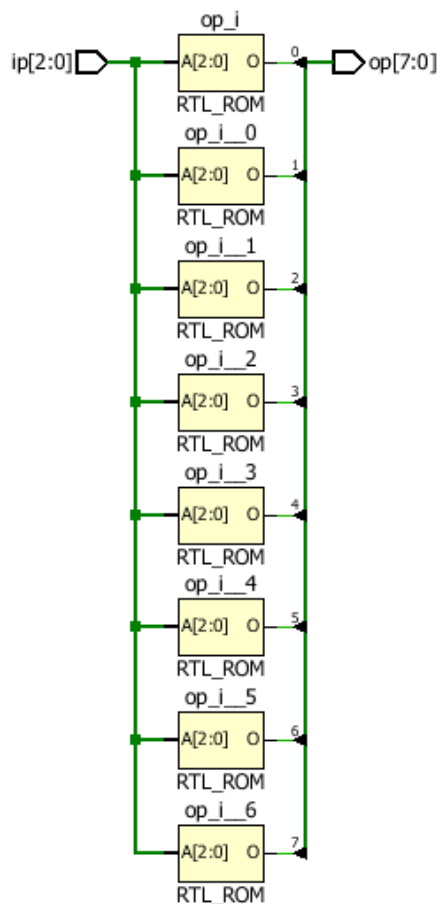

3.TBW Code

entity decoder3_8_df_tbw is

-- Port ();

end decoder3_8_df_tbw;

architecture Behavioral of decoder3_8_df_tbw is

component decoder3_8_df is

Port (ip : in STD_LOGIC_VECTOR (2 downto 0);

op : out STD_LOGIC_VECTOR (7 downto 0));

end component;

signal ip1:STD_LOGIC_VECTOR(2 downto 0):="000";

signal op1:STD_LOGIC_VECTOR(7 downto 0);

begin

uut: decoder3_8_df port map(ip=>ip1,op=>op1);

stim_proc: process

begin

wait for 50ns;

ip1<="000";

wait for 50ns;

```
ip1<="001";
```

```
wait for 50ns;
```

```
ip1<="010";
```

```
wait for 50ns;
```

```
ip1<="011";
```

```
wait for 50ns;
```

```
ip1<="100";
```

```
wait for 50ns;
```

```
ip1<="101";
```

```
wait for 50ns;
```

```
ip1<="110";
```

```
wait for 50ns;
```

```
ip1<="111";
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

4.Waveform



3:8 decoder (Behavioral Model)


1.VHDL Code

```
entity decoder3_8_bv is
  Port ( ip : in STD_LOGIC_VECTOR (2 downto 0);
        op : out STD_LOGIC_VECTOR (7 downto 0));
end decoder3_8_bv;
```

architecture Behavioral of decoder3_8_bv is

```
begin
process(ip)
begin
case ip is
when "000" => op<="00000001";
when "001" => op<="00000010";
when "010" => op<="00000100";
when "011" => op<="00001000";
when "100" => op<="00010000";
when "101" => op<="00100000";
when "110" => op<="01000000";
when "111" => op<="10000000";
when others => NULL;
end case;
end process;
end Behavioral;
```

2.RTL Design

 

3.TBW Code


```

entity decoder3_8_bv_tbw is
-- Port ( );
end decoder3_8_bv_tbw;

architecture Behavioral of decoder3_8_bv_tbw is
component decoder3_8_bv is
    Port ( ip : in STD_LOGIC_VECTOR (2 downto 0);
          op : out STD_LOGIC_VECTOR (7 downto 0));
end component;

signal ip1:STD_LOGIC_VECTOR(2 downto 0):="000";
signal op1:STD_LOGIC_VECTOR(7 downto 0);
begin
uut: decoder3_8_bv port map(ip=>ip1,op=>op1);
stim_proc: process
begin
wait for 50ns;
ip1<="000";

wait for 50ns;
ip1<="001";

wait for 50ns;
ip1<="010";

wait for 50ns;
ip1<="011";

wait for 50ns;
ip1<="100";

wait for 50ns;
ip1<="101";

wait for 50ns;
ip1<="110";

wait for 50ns;
ip1<="111";
wait;
end process;

end Behavioral;

```

4.Waveform



4-bit Comparator (Dataflow Model)

1.VHDL Code


```
entity comparator_4_df is
  Port ( a : in STD_LOGIC_VECTOR (3 downto 0);
        b : in STD_LOGIC_VECTOR (3 downto 0);
        eq : out STD_LOGIC;
        lt : out STD_LOGIC;
        gt : out STD_LOGIC);
end comparator_4_df;
```

architecture Dataflow of comparator_4_df is

```
begin
  eq<='1' when a=b else '0';
  lt<='1' when a<b else '0';
  gt<='1' when a>b else '0';
```

end Dataflow;

2.RTL Design

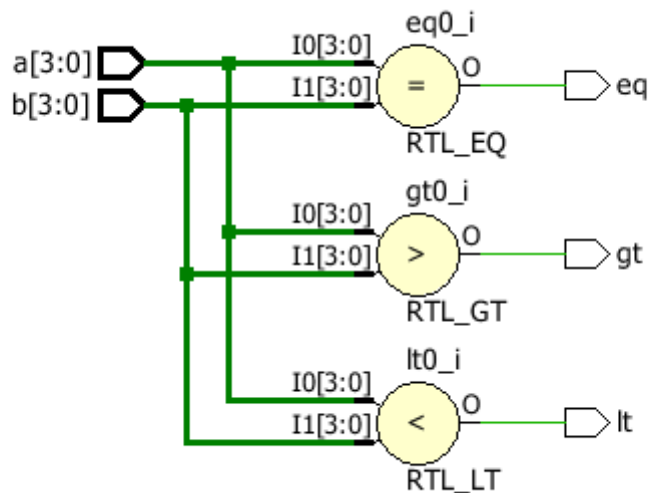

3.TBW Code

```
entity comparator_4_df_tbw is
  -- Port ( );
end comparator_4_df_tbw;
```

architecture Behavioral of comparator_4_df_tbw is
 component comparator_4_df is

```

Port ( a : in STD_LOGIC_VECTOR (3 downto 0);
      b : in STD_LOGIC_VECTOR (3 downto 0);
      eq : out STD_LOGIC;
      lt : out STD_LOGIC;
      gt : out STD_LOGIC);
end component;
signal a1:STD_LOGIC_VECTOR(3 downto 0):="0000";
signal b1:STD_LOGIC_VECTOR(3 downto 0):="0000";
signal eq1:STD_LOGIC;
signal lt1:STD_LOGIC;
signal gt1:STD_LOGIC;
begin
uut: comparator_4_df port map(a=>a1,b=>b1,eq=>eq1,lt=>lt1,gt=>gt1);
stim_proc: process
begin
wait for 100ns;
a1<="0001";
b1<="0001";

wait for 100ns;
a1<="0010";
b1<="0100";


wait for 100ns;
a1<="0100";
b1<="0010";

wait for 100ns;
a1<="0010";
b1<="0010";

wait;
end process;

end Behavioral;
4.Waveform

```

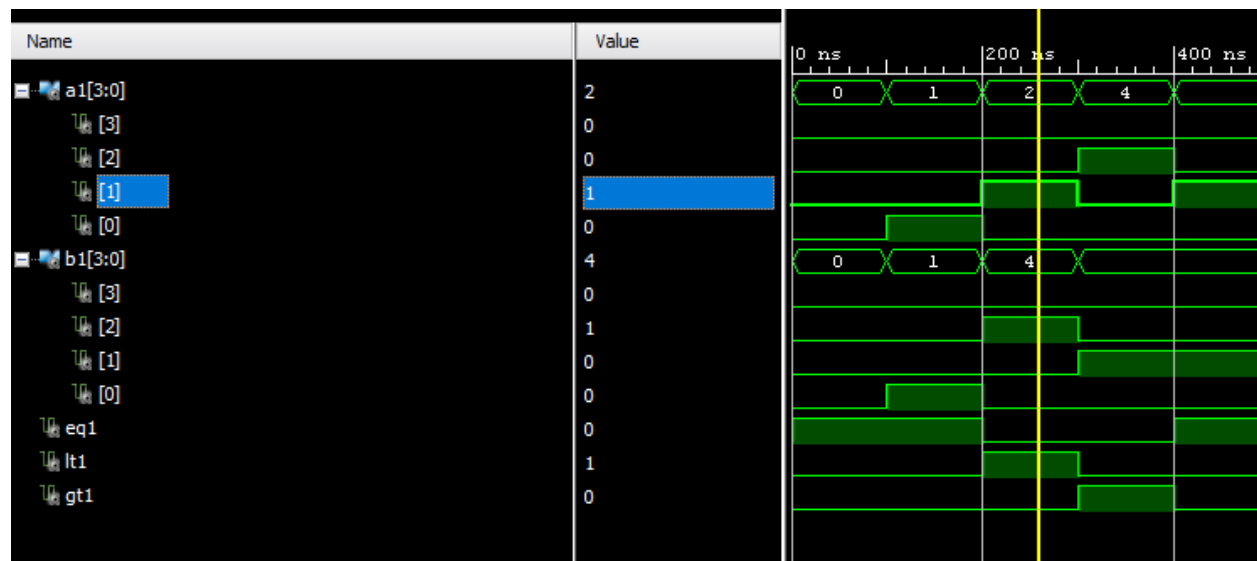


DAY-6

Arithmetic Logic Unit (Behavioral Model)

1.VHDL Design

```
entity alu_bv is
  Port ( a : in UNSIGNED (3 downto 0);
        b : in UNSIGNED (3 downto 0);
        ch : in STD_LOGIC_VECTOR (2 downto 0);
        y : out UNSIGNED (3 downto 0));
end alu_bv;
architecture Behavioral of alu_bv is
begin
  process(a,b,ch)
  begin
    case ch is
      when "000" => y<=a+b;
      when "001" => y<=a-b;
      when "010" => y<=a+"0001";
      when "011" => y<=a-"0001";
      when "100" => y<=a AND b;
      when "101" => y<=a OR b;
      when "110" => y<= NOT a;
      when "111" => y<=a XOR b;
      when others=> null;
    end case;
  end process;
end Behavioral;
```

2.RTL Design

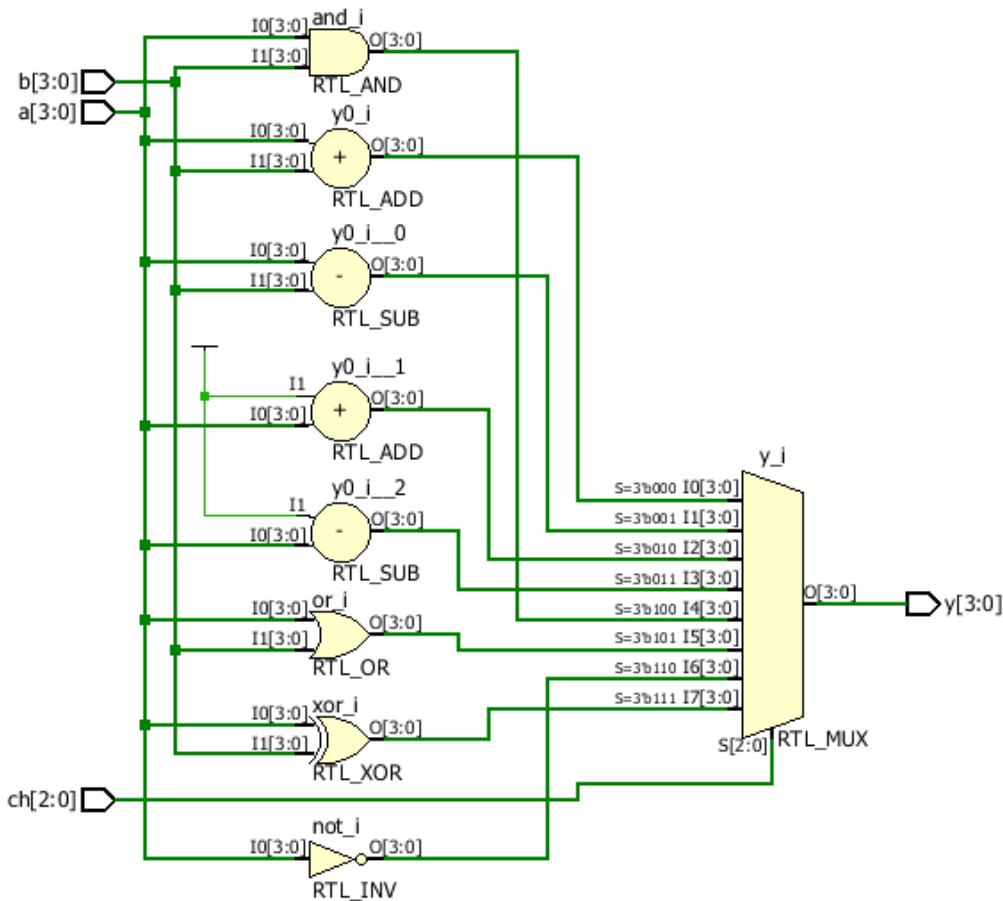

3.TBW Code

entity alu_bv_tbw is

-- Port ();

end alu_bv_tbw;

architecture Behavioral of alu_bv_tbw is

component alu_bv is

Port (a : in UNSIGNED (3 downto 0);

b : in UNSIGNED (3 downto 0);

ch : in STD_LOGIC_VECTOR (2 downto 0);

y : out UNSIGNED (3 downto 0));

end component;

signal a1:UNSIGNED (3 downto 0):="0101";

signal b1:UNSIGNED (3 downto 0):="0011";

signal ch1:STD_LOGIC_VECTOR (2 downto 0):="000";

signal y1:UNSIGNED (3 downto 0);

begin

uut: alu_bv port map(a=>a1,b=>b1,ch=>ch1,y=>y1);

stim_proc: process


begin

```

wait for 50ns;
ch1<="000";
wait for 50ns;
ch1<="001";
wait for 50ns;
ch1<="010";
wait for 50ns;
ch1<="011";
wait for 50ns;
ch1<="100";
wait for 50ns;
ch1<="101";
wait for 50ns;
ch1<="110";
wait for 50ns;
ch1<="111";
wait;
end process;
end Behavioral;

```

4.Waveform

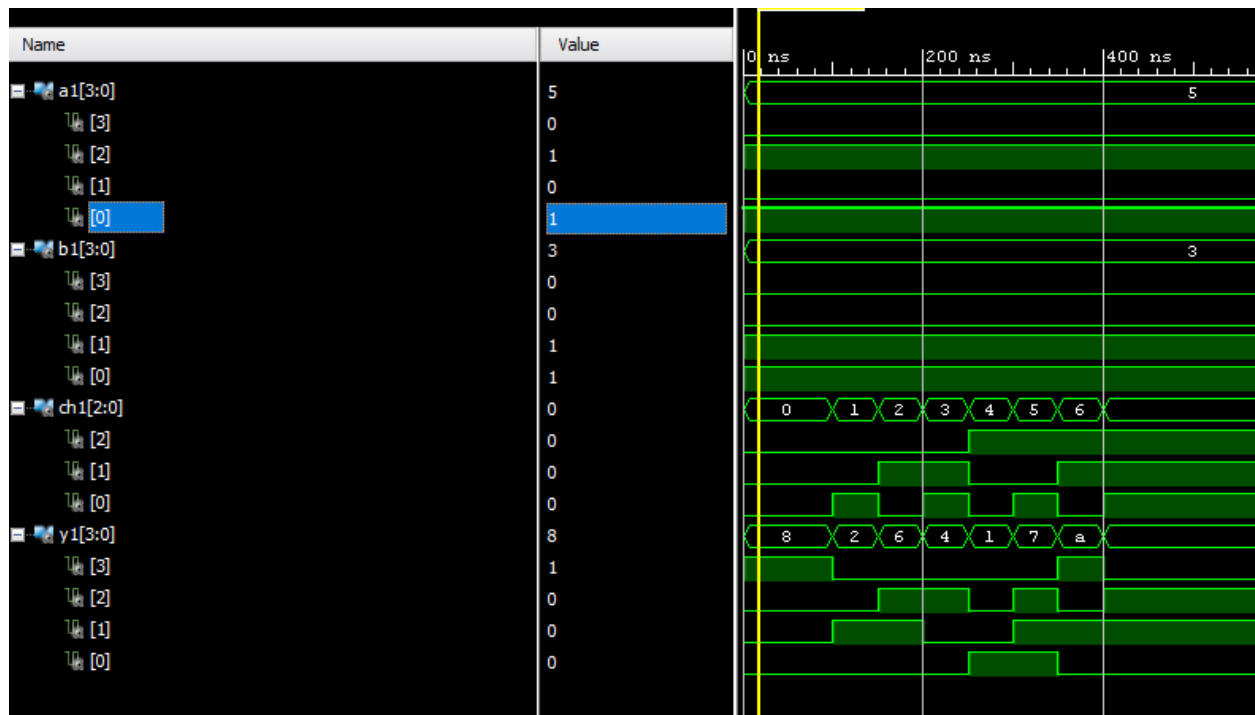

8-bit Parity Checker (Behavioral Model)

1.VHDL Design

entity parity_8 is

Port (a : in STD_LOGIC_VECTOR (7 downto 0);

Po : out STD_LOGIC;

Pe : out STD_LOGIC);

end parity_8;

architecture Behavioral of parity_8 is

begin

process (a)

variable temp:STD_LOGIC;

begin

temp:=a(0) XOR a(1);

for i in 2 to 7 loop

temp:= a(i) XOR temp;

end loop;


Po<=temp;

Pe<= NOT temp;

end process;

end Behavioral;

2.RTL Design

 

3.TBW Code

entity parity_8_tbw is

-- Port ();

end parity_8_tbw;

architecture Behavioral of parity_8_tbw is

component parity_8 is

Port (a : in STD_LOGIC_VECTOR (7 downto 0);

Po : out STD_LOGIC;

Pe : out STD_LOGIC);

end component;

```

signal a1:STD_LOGIC_VECTOR (7 downto 0):="00000000";
signal Po1: STD_LOGIC;
signal Pe1: STD_LOGIC;

begin
  uut: parity_8 port map(a=>a1,Po=>Po1,Pe=>Pe1);
  stim_proc: process
  begin
    --even
    wait for 100 ns;
    a1<="00001111";

    --odd
    wait for 100 ns;
    a1<="00000111";


    --odd
    wait for 100 ns;
    a1<="00000000";

    --even
    wait for 100 ns;
    a1<="11111111";

    wait;
  end process;
end Behavioral;

```

4.Waveform

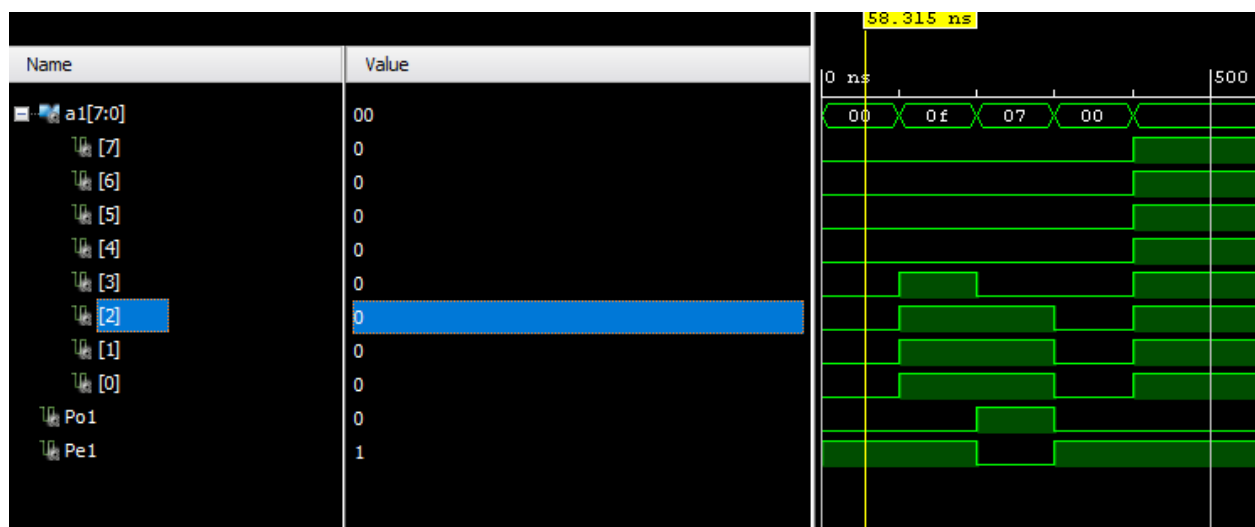

2's Complement (Behavioral Model)

1.VHDL Design


```
use IEEE.NUMERIC_STD.ALL;
entity complement_2 is
  Port ( a : in UNSIGNED (3 downto 0);
        y : out UNSIGNED (3 downto 0));
end complement_2;
```

architecture Behavioral of complement_2 is

```
begin
process(a)
begin
y<=(NOT a) + "0001";
end process;
```

end Behavioral;

2.RTL Design

 

3.TBW Code

```
use IEEE.NUMERIC_STD.ALL;
entity complement_2_tbw is
-- Port ( );
end complement_2_tbw;
```

architecture Behavioral of complement_2_tbw is

component complement_2 is

```
  Port ( a : in UNSIGNED (3 downto 0);
        y : out UNSIGNED (3 downto 0));
end component;
```

end component;

signal a1:UNSIGNED (3 downto 0):="0000";


signal y1:UNSIGNED (3 downto 0);

```

begin
  uut: complement_2 port map(a=>a1,y=>y1);
  stim_proc: process
  begin
    wait for 100 ns;
    a1<="0111";
    wait for 100 ns;
    a1<="0001";
    wait for 100 ns;
    a1<="1001";
    wait for 100 ns;
    a1<="1101";
    wait;
  end process;
end Behavioral;

```

4.Waveform

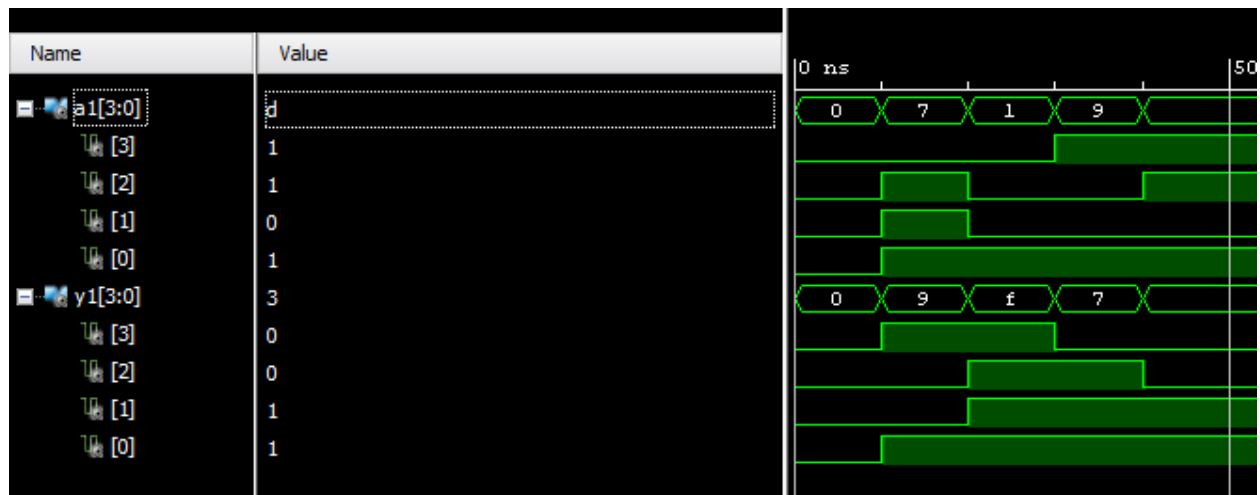

DAY 7


Full Adder (Structural Model)

1.VHDL Design

```
entity fulladder_str is
    Port ( x : in STD_LOGIC;
          y : in STD_LOGIC;
          z : in STD_LOGIC;
          sum : out STD_LOGIC;
          carry : out STD_LOGIC);
end fulladder_str;

architecture Structural of fulladder_str is
    component ord is
        Port ( a : in STD_LOGIC;
              b : in STD_LOGIC;
              c : out STD_LOGIC);
    end component;
    component half_adderdf is
        Port ( x : in STD_LOGIC;
              y : in STD_LOGIC;
              s : out STD_LOGIC;
              c : out STD_LOGIC);
    end component;
    signal s1,c1,c2:STD_LOGIC;
begin
    l1:half_adderdf port map (x,y,s1,c1);
    l2:half_adderdf port map(s1,z,sum,c2);
    l3:ord port map(c1,c2,carry);
end Structural;
```

2.RTL Design

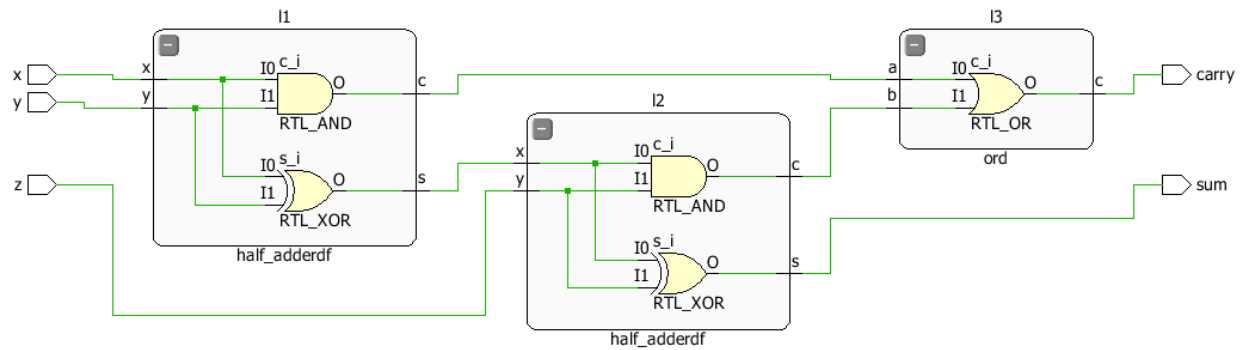

3.TBW Code

entity fulladder_str_tbw is

-- Port ();

end fulladder_str_tbw;

architecture Behavioral of fulladder_str_tbw is

component fulladder_str is

Port (x : in STD_LOGIC;

y : in STD_LOGIC;

z : in STD_LOGIC;

sum : out STD_LOGIC;

carry : out STD_LOGIC);

end component;

signal x1: STD_LOGIC:='0';

signal y1: STD_LOGIC:='0';

signal z1: STD_LOGIC:='0';

signal sum1: STD_LOGIC;

signal carry1: STD_LOGIC;

begin

uut: fulladder_str port map(x=>x1,y=>y1,z=>z1,sum=>sum1,carry=>carry1);

stim_proc: process

begin

wait for 50 ns;

x1<='0';

y1<='0';

z1<='0';

wait for 50 ns;

x1<='0';

y1<='0';

z1<='1';


wait for 50 ns;

```

x1<='0';
y1<='1';
z1<='0';
wait for 50 ns;
x1<='0';
y1<='1';
z1<='1';
wait for 50 ns;
x1<='1';
y1<='0';
z1<='0';
wait for 50 ns;
x1<='1';
y1<='0';
z1<='1';
wait for 50 ns;
x1<='1';
y1<='1';
z1<='0';
wait for 50 ns;
x1<='1';
y1<='1';
z1<='1';
wait;
end process;
end Behavioral;

```

4.Waveform

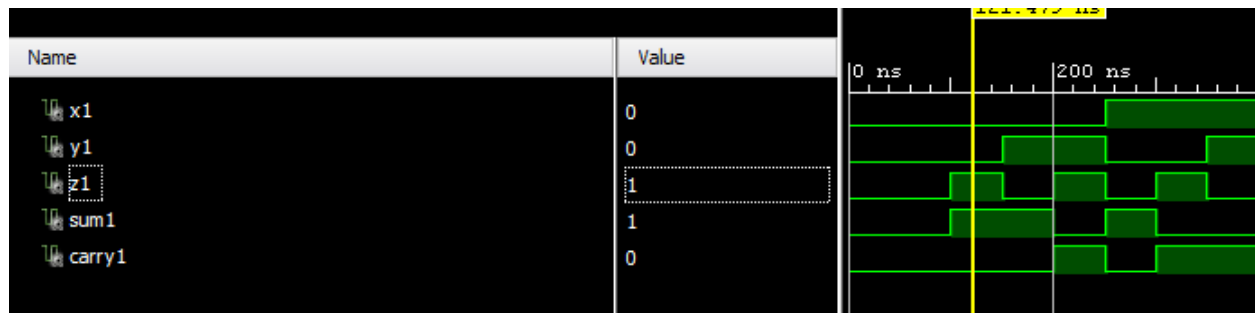

4-bit Ripple Carry Adder (Structural Model)

1.VHDL Design

entity ripple_carry is

```
Port ( a : in STD_LOGIC_VECTOR (3 downto 0);  
      b : in STD_LOGIC_VECTOR (3 downto 0);  
      cin : in STD_LOGIC;  
      sum : out STD_LOGIC_VECTOR (3 downto 0);  
      cout : out STD_LOGIC);
```

end ripple_carry;

architecture Structural of ripple_carry is

component full_adder_df is

```
Port ( x : in STD_LOGIC;  
      y : in STD_LOGIC;  
      z : in STD_LOGIC;  
      s : out STD_LOGIC;  
      c : out STD_LOGIC);
```

end component;


signal c0,c1,c2:STD_LOGIC;

begin

```
l1:full_adder_df port map (a(0),b(0),cin,sum(0),c0);  
l2:full_adder_df port map (a(1),b(1),c0,sum(1),c1);  
l3:full_adder_df port map (a(2),b(2),c1,sum(2),c2);  
l4:full_adder_df port map (a(3),b(3),c2,sum(3),cout);
```

end Structural;

2.RTL Design

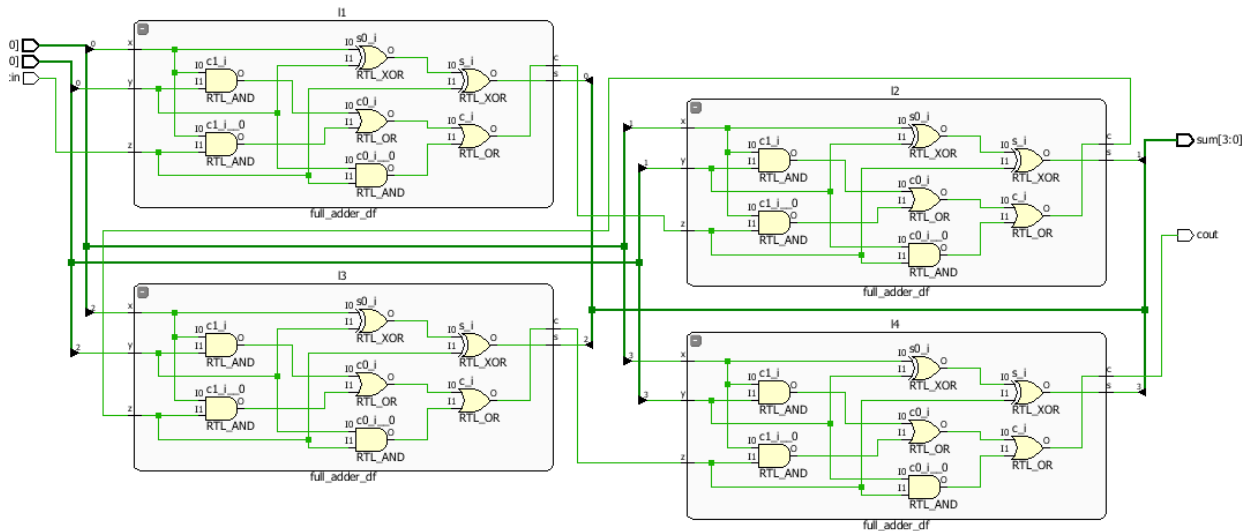

3.TBW Code

entity ripple_carry_tbw is

-- Port ();

end ripple_carry_tbw;

architecture Behavioral of ripple_carry_tbw is

component ripple_carry is

```
Port ( a : in STD_LOGIC_VECTOR (3 downto 0);
      b : in STD_LOGIC_VECTOR (3 downto 0);
      cin : in STD_LOGIC;
      sum : out STD_LOGIC_VECTOR (3 downto 0);
      cout : out STD_LOGIC);
```

end component;

```
signal a1: STD_LOGIC_VECTOR (3 downto 0):="0000";
```

```
signal b1: STD_LOGIC_VECTOR (3 downto 0):="0000";
```

```
signal cin1: STD_LOGIC:='0';
```

```
signal sum1: STD_LOGIC_VECTOR (3 downto 0);
```

```
signal cout1: STD_LOGIC;
```

begin

```
uut: ripple_carry port map(a=>a1,b=>b1,cin=>cin1,sum=>sum1,cout=>cout1);
```

stim_proc: process

begin

```
wait for 50 ns;
```

```
a1<="0000";
```

```
b1<="0000";
```

```
cin1<='0';
```

```
wait for 50 ns;
a1<="0001";
b1<="0001";
cin1<='0';
```

```
wait for 50 ns;
a1<="0111";
b1<="0001";
cin1<='1';
```

```
wait for 50 ns;
a1<="1010";
b1<="0010";
cin1<='1';
```

```
wait;
end process;
end Behavioral;
```

4.Waveform



Adder-Subtractor Composite Unit (Structural Model)

1.VHDL Design

```
entity add_sub_comp is
  Port ( a : in STD_LOGIC_VECTOR (3 downto 0);
        b : in STD_LOGIC_VECTOR (3 downto 0);
        cin : in STD_LOGIC;
        sum : out STD_LOGIC_VECTOR (3 downto 0);
        cout : out STD_LOGIC);
end add_sub_comp;

architecture Structural of add_sub_comp is


  component full_adder_df is
    Port ( x : in STD_LOGIC;
          y : in STD_LOGIC;
          z : in STD_LOGIC;
          s : out STD_LOGIC;
          c : out STD_LOGIC);
  end component;

  signal c0,c1,c2:STD_LOGIC;
  signal temp:STD_LOGIC_VECTOR(3 downto 0);
  begin
    gk:for i in 0 to 3 generate
      temp(i)<=b(i) XOR cin;
    end generate;

    l1:full_adder_df port map (a(0),temp(0),cin,sum(0),c0);
    l2:full_adder_df port map (a(1),temp(1),c0,sum(1),c1);
    l3:full_adder_df port map (a(2),temp(2),c1,sum(2),c2);
    l4:full_adder_df port map (a(3),temp(3),c2,sum(3),cout);

  end Structural;
```

2.RTL Design

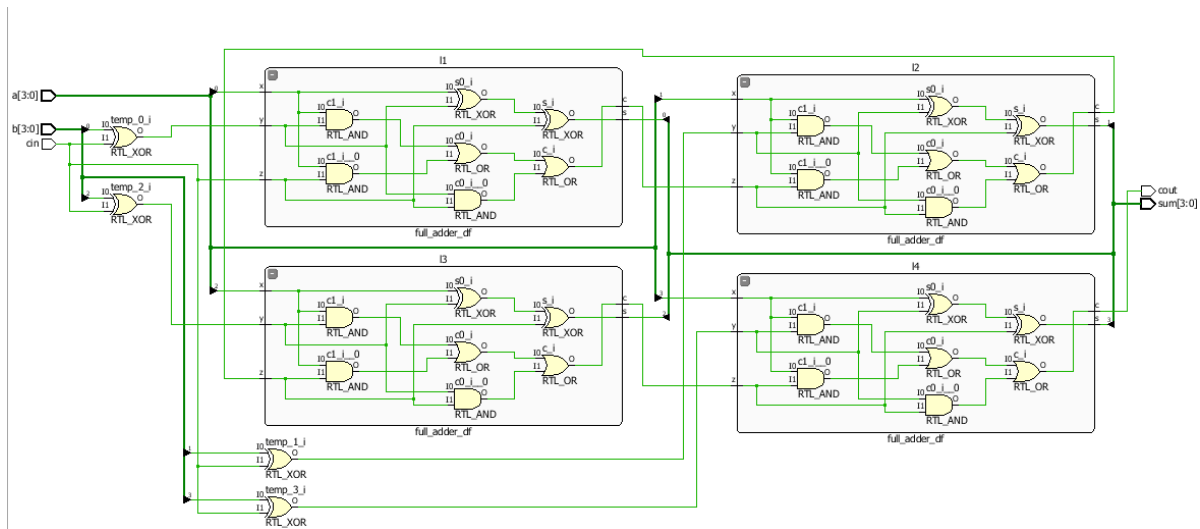

3.TBW Code

entity add_sub_comp_tbw is

-- Port ();

end add_sub_comp_tbw;

architecture Behavioral of add_sub_comp_tbw is

component add_sub_comp is

Port (a : in STD_LOGIC_VECTOR (3 downto 0);
b : in STD_LOGIC_VECTOR (3 downto 0);
cin : in STD_LOGIC;
sum : out STD_LOGIC_VECTOR (3 downto 0);
cout : out STD_LOGIC);

end component;

signal a1: STD_LOGIC_VECTOR (3 downto 0):="0000";

signal b1: STD_LOGIC_VECTOR (3 downto 0):="0000";

signal cin1: STD_LOGIC:='0';

signal sum1: STD_LOGIC_VECTOR (3 downto 0);

signal cout1: STD_LOGIC;

begin

uut: add_sub_comp port map(a=>a1,b=>b1,cin=>cin1,sum=>sum1,cout=>cout1);

stim_proc: process

begin

wait for 50 ns;

a1<="0000";

b1<="0000";

cin1<='0';

wait for 50 ns;

```

a1<="0001";
b1<="0001";
cin1<='0';

```

```

wait for 50 ns;
a1<="0111";
b1<="0001";
cin1<='1';

```

```

wait for 50 ns;
a1<="1010";
b1<="0010";
cin1<='1';

```

```

wait;
end process;
end Behavioral;

```

4.Waveform



8:1 MUX (Structural Model)

1.VHDL Design

entity mux8_1 is

```
    Port ( ip : in STD_LOGIC_VECTOR (7 downto 0);  
          sel : in STD_LOGIC_VECTOR (2 downto 0);  
          y : out STD_LOGIC);
```

end mux8_1;

architecture Structural of mux8_1 is

component mux4_1_df is

```
    Port ( ip : in STD_LOGIC_VECTOR (3 downto 0);  
          sel : in STD_LOGIC_VECTOR (1 downto 0);  
          y : out STD_LOGIC);
```

end component;

component mux2_1 is

```
    Port ( a : in STD_LOGIC;  
          b : in STD_LOGIC;  
          c : out STD_LOGIC;  
          s : in STD_LOGIC);
```

end component;

signal x1,x2:STD_LOGIC;

begin


l1:mux4_1_df port map(ip(7 downto 4),sel(1 downto 0),x1);

l2:mux4_1_df port map(ip(3 downto 0),sel(1 downto 0),x2);

l3:mux2_1 port map(x2,x1,y,sel(2));

end Structural;

2.RTL Design

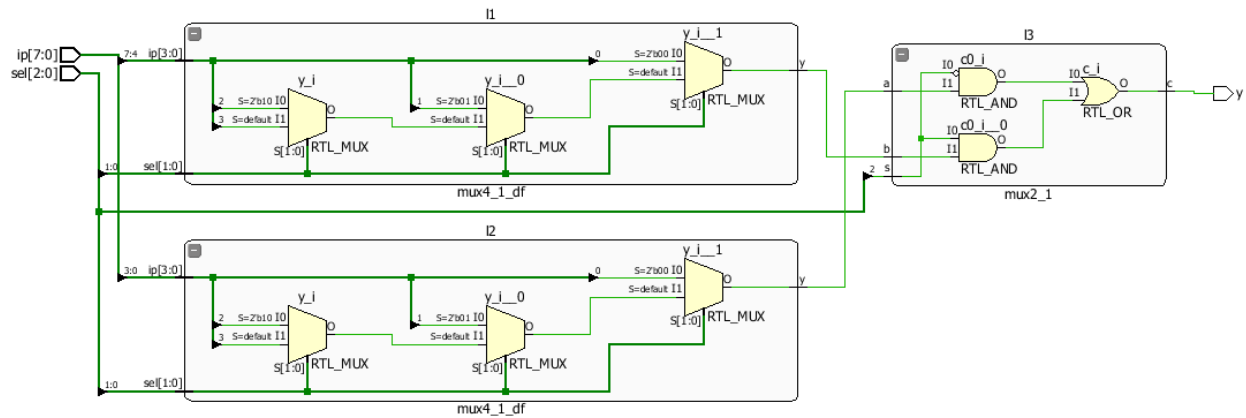

3.TBW Code

entity mux8_1_tbw is

-- Port ();

end mux8_1_tbw;

architecture Behavioral of mux8_1_tbw is

component mux8_1 is

Port (ip : in STD_LOGIC_VECTOR (7 downto 0);

sel : in STD_LOGIC_VECTOR (2 downto 0);

y : out STD_LOGIC);

end component;

signal ip1:STD_LOGIC_VECTOR(7 downto 0):="01010101";

signal sel1:STD_LOGIC_VECTOR(2 downto 0):="000";

signal y1:STD_LOGIC;

begin

uut:mux8_1 port map(ip=>ip1,sel=>sel1,y=>y1);

stim_proc:process

begin

wait for 50 ns;

sel1<="000";

wait for 50 ns;

sel1<="001";

wait for 50 ns;

sel1<="010";

wait for 50 ns;

sel1<="011";

```
wait for 50 ns;  
sel1<="100";
```

```
wait for 50 ns;  
sel1<="101";
```

```
wait for 50 ns;  
sel1<="110";
```

```
wait for 50 ns;  
sel1<="111";
```

```
wait;  
end process;  
end Behavioral;
```

4.Waveform



DAY 8

SR Flip-Flop (Behavioral Model)

1.VHDL Design

entity sr_ff is

```
Port ( s : in STD_LOGIC;  
      r : in STD_LOGIC;  
      clk : in STD_LOGIC;  
      q : out STD_LOGIC;  
      qn : out STD_LOGIC);
```

end sr_ff;

architecture Behavioral of sr_ff is

begin

process(s,r,clk)

begin

if (clk'event and clk='1') then

if(s='0' and r='1') then

q<='0';

qn<='1';

elsif(s='1' and r='0') then

q<='1';

qn<='0';

elsif(s='1' and r='1') then

q<='X';

qn<='X';


end if;

end if;

end process;

end Behavioral;

2.RTL Design

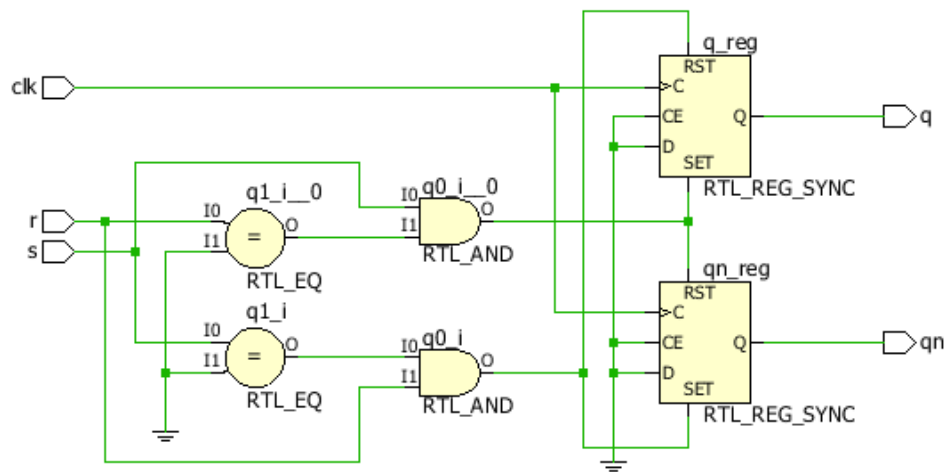

3.TBW Code

```
entity ss_ff_tbw is
```

```
-- Port ( );
```

```
end ss_ff_tbw;
```

```
architecture Behavioral of ss_ff_tbw is
```

```
component sr_ff is
```

```
Port ( s : in STD_LOGIC;
```

```
      r : in STD_LOGIC;
```

```
      clk : in STD_LOGIC;
```

```
      q : out STD_LOGIC;
```

```
      qn : out STD_LOGIC);
```

```
end component;
```

```
constant clock_period:time:=60 ns;
```

```
signal s1:STD_LOGIC:='0';
```

```
signal r1:STD_LOGIC:='0';
```

```
signal clk1:STD_LOGIC:='0';
```

```
signal q1:STD_LOGIC;
```

```
signal qn1:STD_LOGIC;
```

```
begin
```

```
  uut: sr_ff port map(s=>s1,r=>r1,clk=>clk1,q=>q1,qn=>qn1);
```

```
  clk1<=not clk1 after clock_period/2;
```

```
  stim_proc:process
```

```
  begin
```

```
    wait for 100 ns;
```

```
    s1<='0';
```

```
    r1<='1';
```

```
  wait for 100 ns;
```

```
  s1<='0';
```

```
  r1<='0';
```

```

wait for 100 ns;
s1<='1';
r1<='0';
wait for 100 ns;
s1<='1';
r1<='1';

```

```

wait;
end process;


```

```

end Behavioral;

```

4.Waveform

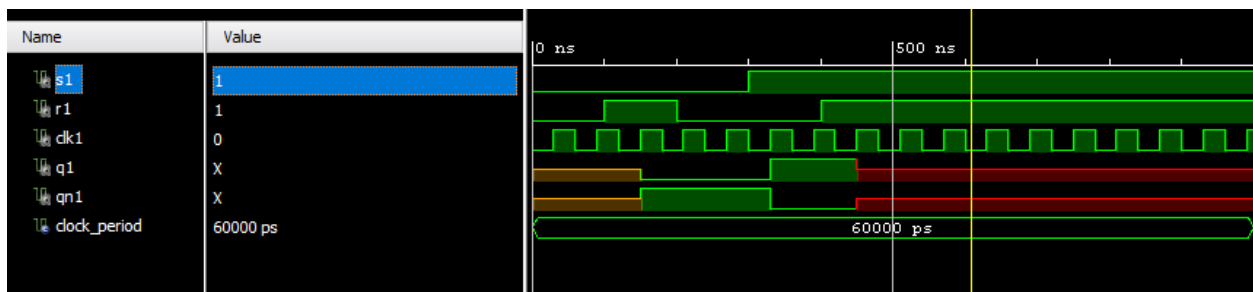


JK Flip-Flop (Behavioral Model)

1.VHDL Design

```
entity jk_ff is
  Port ( j : in STD_LOGIC;
        k : in STD_LOGIC;
        clk : in STD_LOGIC;
        q : out STD_LOGIC;
        qn : out STD_LOGIC);
end jk_ff;
architecture Behavioral of jk_ff is
  signal temp : STD_LOGIC := '0';
begin
  process(clk)
  begin
    if (clk'event and clk = '1') then
      if (j = '0' and k = '1') then
        temp <= '0'; -- Reset
      elsif (j = '1' and k = '0') then
        temp <= '1'; -- Set
      elsif (j = '1' and k = '1') then
        temp <= not temp; -- Toggle
      end if; -- (j=0 and k=0): Hold -> do nothing
    end if;
  end process;
  q <= temp;
  qn <= not temp;
end Behavioral;
```

2.RTL Design

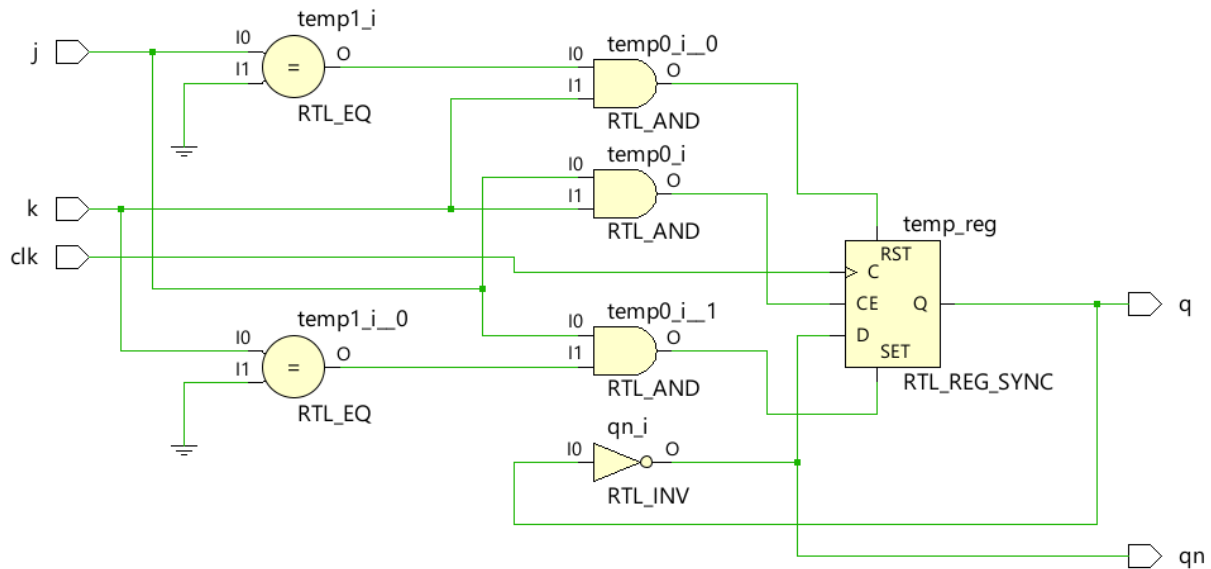

3.TBW Code

entity **jk_ff_tbw** is

-- Port ();

end **jk_ff_tbw**;

architecture Behavioral of **jk_ff_tbw** is

component **jk_ff** is

Port (**j** : in **STD_LOGIC**;

k : in **STD_LOGIC**;

clk : in **STD_LOGIC**;

q : inout **STD_LOGIC**;

qn : inout **STD_LOGIC**);

end component;

constant **clock_period**:time:=60 ns;

signal **j1**:**STD_LOGIC**:= '0';

signal **k1**:**STD_LOGIC**:= '0';

signal **clk1**:**STD_LOGIC**:= '0';

signal **q1**:**STD_LOGIC**;

signal **qn1**:**STD_LOGIC**;

begin

uut: **jk_ff** port map(**j**=>**j1**,**k**=>**k1**,**clk**=>**clk1**,**q**=>**q1**,**qn**=>**qn1**);

clk1 <= not **clk1** after **clock_period**/2;

stim_proc:process

begin


wait for 100 ns;

```

j1<='0';
k1<='1';
wait for 100 ns;
j1<='0';
k1<='0';
wait for 100 ns;
j1<='1';
k1<='0';
wait for 100 ns;
j1<='1';
k1<='1';
wait;
end process;
end Behavioral;

```

4.Waveform

 


D Flip-Flop (Behavioral Model)

1.VHDL Design

```
entity d_ff is
  Port ( d : in STD_LOGIC;
        clk : in STD_LOGIC;
        q : inout STD_LOGIC);
end d_ff;
architecture Behavioral of d_ff is
begin
  process(d,clk)
  begin
    if(clk'event and clk='1') then
      q<=d;
    end if;
  end process;
end Behavioral;
```

2.RTL Design

 

3.TBW Code


```
entity d_ff_tbw is
-- Port ( );
end d_ff_tbw;
architecture Behavioral of d_ff_tbw is
  component d_ff is
    Port ( d : in STD_LOGIC;
          clk : in STD_LOGIC;
          q : inout STD_LOGIC);
  end component;
end component;
```

```

constant clock_period:time:=60 ns;
signal d1:STD_LOGIC:='0';
signal clk1:STD_LOGIC:='0';
signal q1:STD_LOGIC;
begin
uut: d_ff port map(d=>d1,clk=>clk1,q=>q1);
clk1<=not clk1 after clock_period/2;
stim_proc:process
begin
wait for 100 ns;
d1<='1';
wait for 100 ns;
d1<='0';
wait;
end process;
end Behavioral;

```

4.Waveform

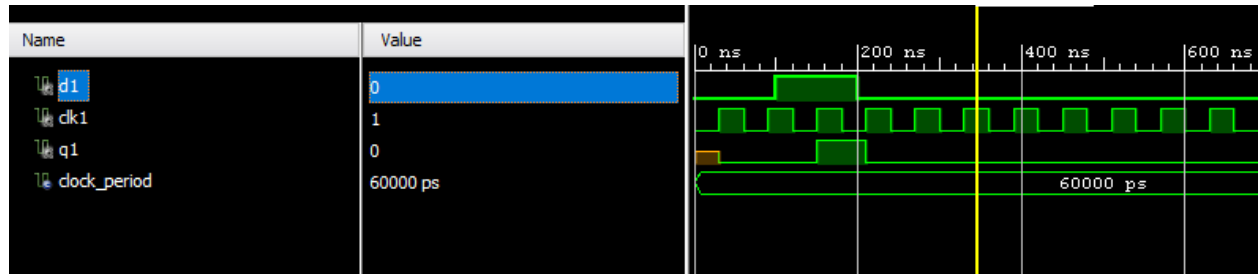


T Flip-Flop (Behavioral Model)

1.VHDL Design

```
entity t_ff is
  Port (
    t : in STD_LOGIC;
    clk : in STD_LOGIC;
    q : out STD_LOGIC
  );
end t_ff;
architecture Behavioral of t_ff is
  signal temp : STD_LOGIC := '0';
begin
  process(clk)
  begin
    if(clk'event and clk='1') then
      if t = '1' then
        temp <= not temp;
      end if;
    end if;
  end process;
  q <= temp;
end Behavioral;
```

2.RTL Design

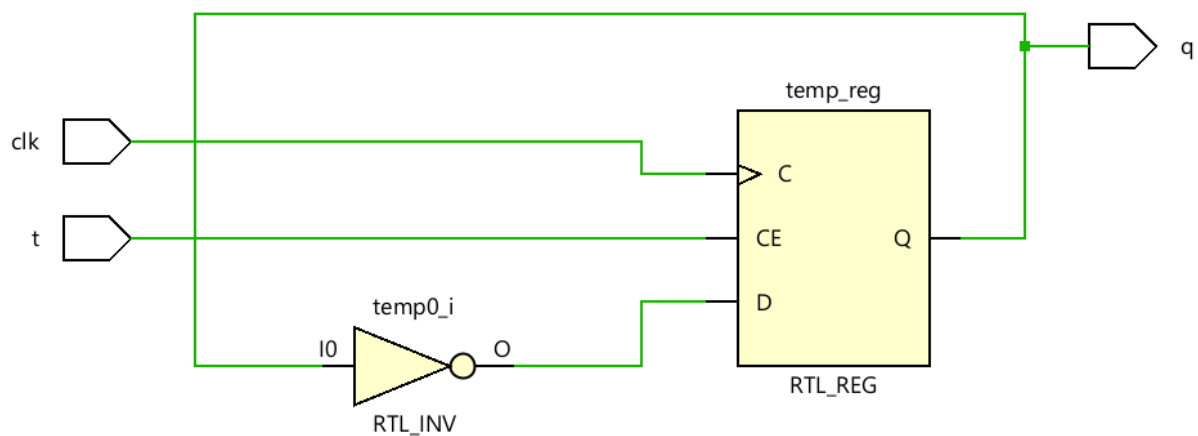

3.TBW Code

```
entity t_ff_tbw is
  -- Port ( );
```

```
end t_ff_tbw;
```

architecture Behavioral of t_ff_tbw is

component t_ff is

Port (t : in STD_LOGIC;

clk : in STD_LOGIC;

q : out STD_LOGIC);

end component;

constant clock_period:time:=60 ns;

signal t1:STD_LOGIC:='0';

signal clk1:STD_LOGIC:='0';

signal q1:STD_LOGIC;

begin

uut: t_ff port map(t=>t1,clk=>clk1,q=>q1);

clk1<=not clk1 after clock_period/2;

stim_proc:process

begin

wait for 100 ns;

t1<='0';

wait for 100 ns;


t1<='1';

wait;

end process;

end Behavioral;

4.Waveform

 

4-bit Shift Register (Structural Model)

1.VHDL Design

entity shift_register is

Port (ip : in STD_LOGIC;

clk : in STD_LOGIC;

op : inout STD_LOGIC_VECTOR (3 downto 0));

end shift_register;

architecture Structural of shift_register is

component d_ff is

Port (d : in STD_LOGIC;

clk : in STD_LOGIC;

q : inout STD_LOGIC);

end component;

begin

l1: d_ff port map(ip,clk,op(0));


l2: d_ff port map(op(0),clk,op(1));

l3: d_ff port map(op(1),clk,op(2));

l4: d_ff port map(op(2),clk,op(3));

end Structural;

2.RTL Design

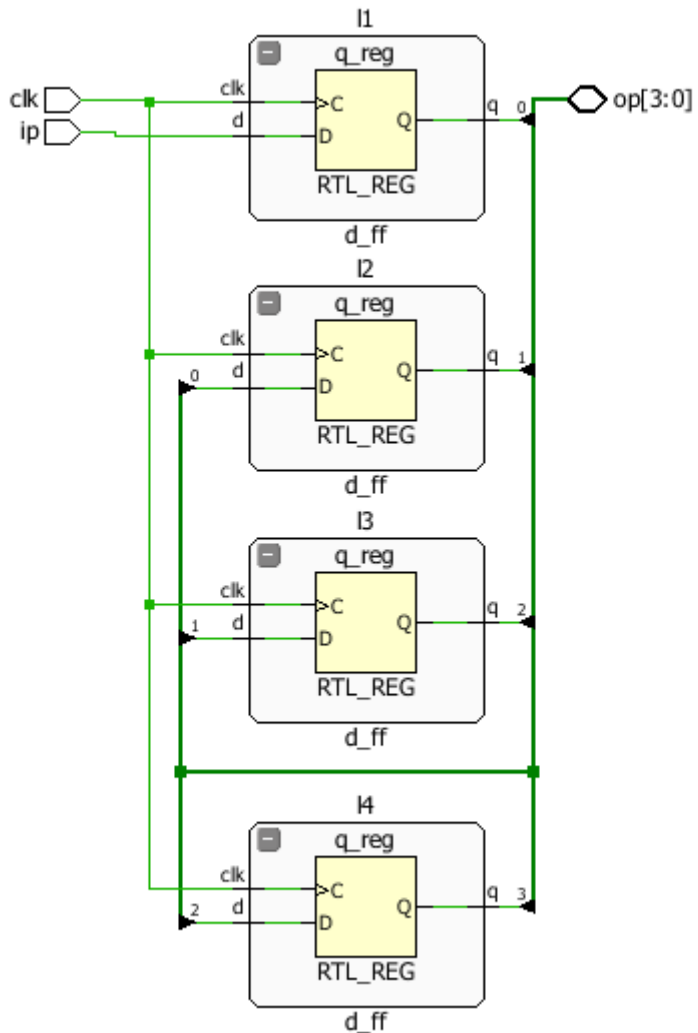

3.TBW Code

```
entity shift_register_tbw is
-- Port ( );
end shift_register_tbw;
architecture Behavioral of shift_register_tbw is
component shift_register is
Port ( ip : in STD_LOGIC;
      clk : in STD_LOGIC;
      op : inout STD_LOGIC_VECTOR (3 downto 0));
end component;
constant clock_period:time:=60 ns;
```

```

signal ip1:STD_LOGIC:='0';
signal clk1:STD_LOGIC:='0';
signal op1:STD_LOGIC_VECTOR(3 downto 0);
begin
  uut: shift_register port map(ip=>ip1,clk=>clk1,op=>op1);
  clk1<=not clk1 after clock_period/2;
  stim_proc:process
  begin
    wait for 100 ns;
    ip1<='1';
    wait;
  end process;
end Behavioral;

```

4.Waveform




DAY 9

4-bit Up Counter (Behavioral Model)

1.VHDL Design

```
use IEEE.NUMERIC_STD.ALL;
entity bitup_4 is
  Port ( clr : in STD_LOGIC;
        clk : in STD_LOGIC;
        q : out unsigned(3 downto 0));
end bitup_4;
architecture Behavioral of bitup_4 is
  signal temp:unsigned(3 downto 0):="0000";
begin
  process(clr,clk)
  begin
    if(clr='1') then
      temp<="0000";
    else
      if (clk'event and clk='1') then
        temp<=temp+"0001";
      end if;
    end if;
    q<=temp;
  end process;
end Behavioral;
```


2.RTL Design

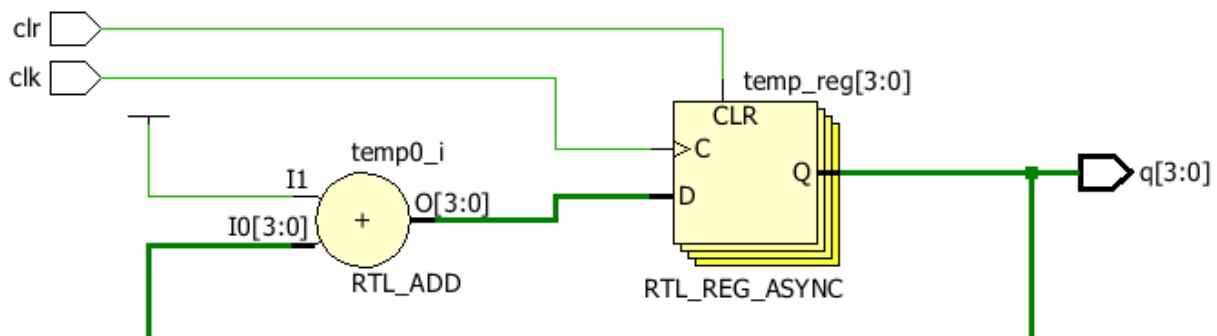

3.TBW Code

```
entity bit4_up_tbw is
-- Port ( );
end bit4_up_tbw;
architecture Behavioral of bit4_up_tbw is
component bitup_4 is
    Port ( clr : in STD_LOGIC;
          clk : in STD_LOGIC;
          q : out unsigned(3 downto 0));
end component;
constant clock_period:time:=60 ns;
signal clr1:STD_LOGIC:='0';
signal clk1:STD_LOGIC:='0';
signal q1:UNSIGNED(3 downto 0);
begin
    uut: bitup_4 port map(clr=>clr1,clk=>clk1,q=>q1);
    clk1<=not clk1 after clock_period/2;
    stim_proc:process
    begin
        wait for 50 ns;
        clr1<='1';
        wait for 100 ns;
        clr1<='0';
        wait;
    end process;
end Behavioral;
```

4.Waveform

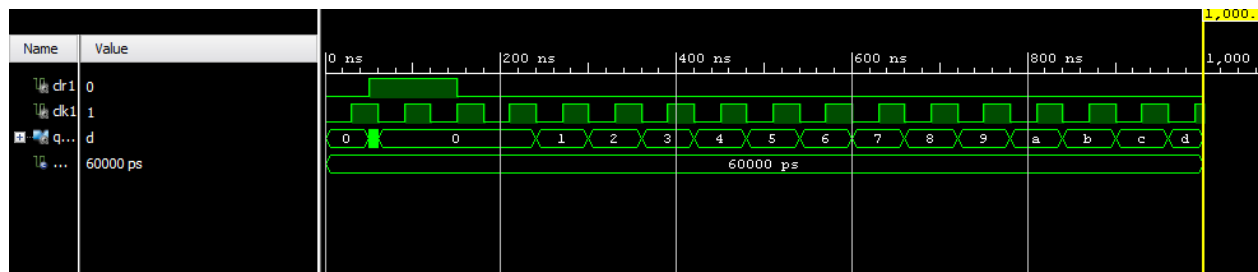


4-bit Down Counter (Behavioral Model)

1.VHDL Design

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity bit4_down is
  Port ( clr : in STD_LOGIC;
        clk : in STD_LOGIC;
        q : out unsigned (3 downto 0));
end bit4_down;

architecture Behavioral of bit4_down is
  signal temp:unsigned (3 downto 0):="0000";
begin
  process(clr,clk)
  begin
    if(clr='1') then
      temp<="1111";
    else
      if (clk'event and clk='1') then
        temp<=temp-"0001";
      end if;
    end if;
    q<=temp;
  end process;
end Behavioral;
```

2.RTL Design

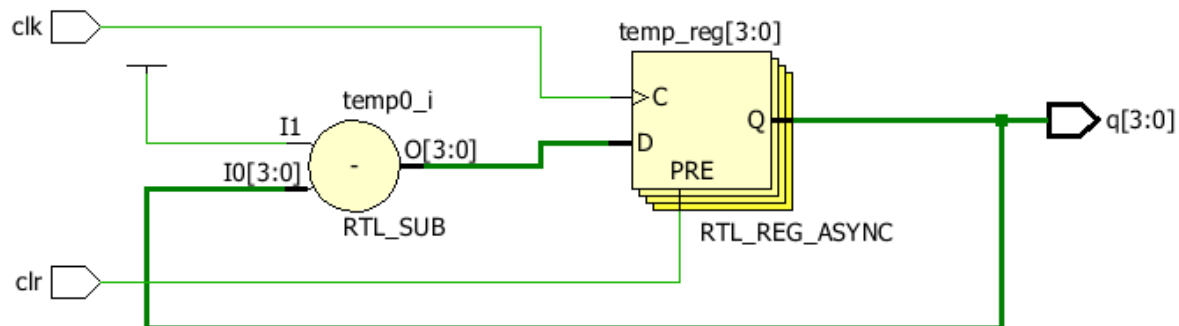

3.TBW Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity bit4_down_tbw is
-- Port ( );
end bit4_down_tbw;
```

architecture Behavioral of bit4_down_tbw is

component bit4_down is

```
Port ( clr : in STD_LOGIC;
      clk : in STD_LOGIC;
      q : out unsigned (3 downto 0));
```

end component;

```
constant clock_period:time:=60 ns;
```

```
signal clr1:STD_LOGIC:='0';
```

```
signal clk1:STD_LOGIC:='0';
```

```
signal q1:UNSIGNED(3 downto 0);
```

```
begin
```

```
uut: bit4_down port map(clr=>clr1,clk=>clk1,q=>q1);
```

```
clk1<=not clk1 after clock_period/2;
```

```
stim_proc:process
```

```
begin
```

```
wait for 50 ns;
```

```
clr1<='1';
```

```
wait for 80 ns;
```

```
clr1<='0';
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

4.Waveform

